

Chapter 12

Standard Blocks: Registers

SKEE1223 Digital Electronics

Mun'im/Arif/Izam

FKE, Universiti Teknologi Malaysia

December 8, 2015



- 1 Overview
- 2 Registers
- 3 Shift Registers
- 4 Shift Register Chips
- 5 Shift Register Counters

Sequential MSI

- Sequential MSI circuits are based on flip-flops.
- **Register:**
 - A register is a memory device that can be used to store more than one bit of information.
- **Counter:**
 - A register that is capable of incrementing or decrementing its contents.
- **Shift register:**
 - A register that shifts data from one flip-flop to the next

Register

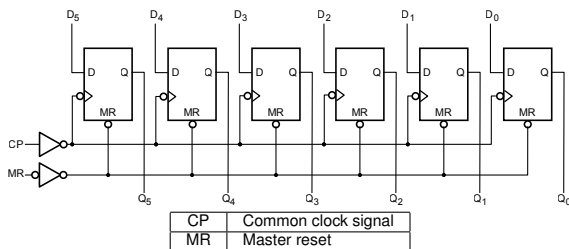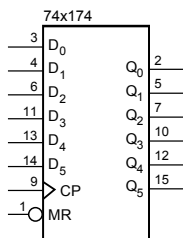
- Usually realized as several flip-flops with common control signals that control the movement of data to and from the register.




Shift Registers

- Shift register: a register which can shift data left or right when a shift signal is applied.
- All flip-flops are driven by a common clock and common reset.
- Applications:
 - Producing time delay
 - Converting data from parallel to serial or vice versa.

Data Movement in Shift Registers

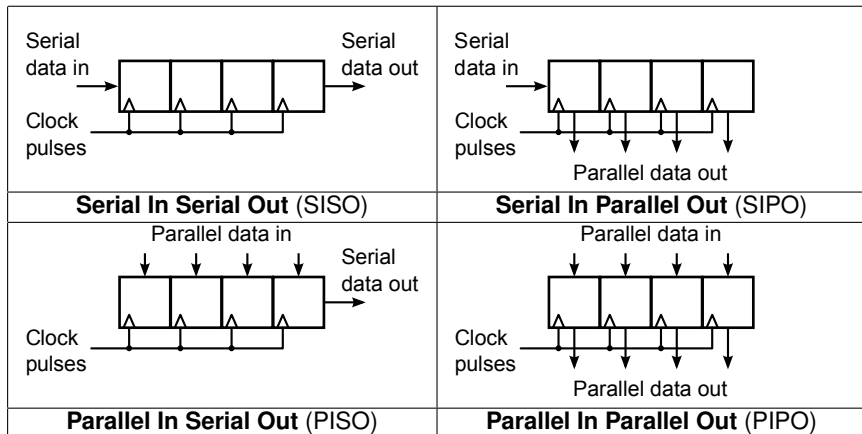


A 4-bit SIPO Shift Register

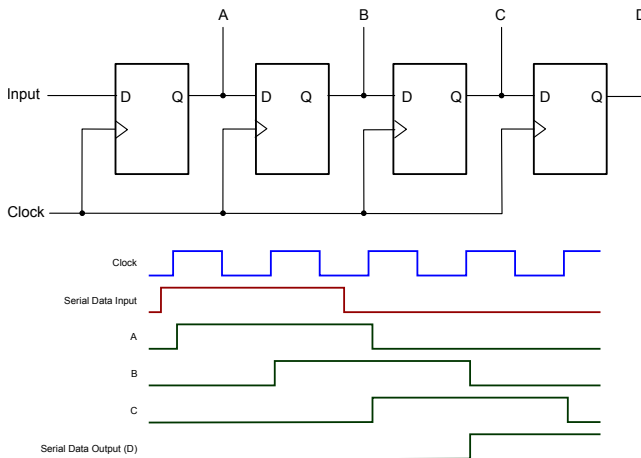

Because of propagation delay, the value loaded into FF is the value of input before rising clock edge.


Shift Register Animation

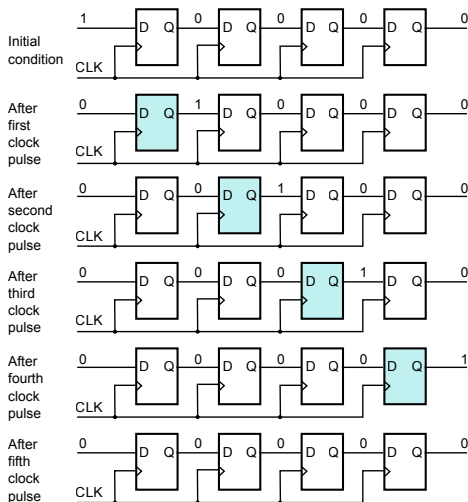

Behavior of SIPO shift register in tabular form


Clock #	Input	A+	B+	C+	D+
0	1	1	0	0	0
1	1	1	1	0	0
2	0	1	1	1	0
3	0	0	1	1	1
4	0	0	0	1	1
5	1	0	0	0	1
6	0	1	0	0	0

A More Practical SIPO Shift Register

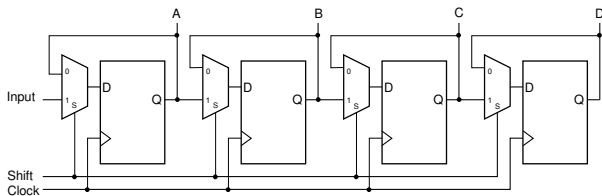

Shift = 0	Hold mode
Shift = 1	Shift mode

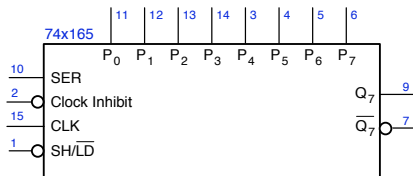
74x165 Parallel Load 8-bit Shift Register IC



SER	Serial data input
SH/LD	1 = shift, 0 = load
P0-P7	Parallel data inputs
Q7	Output of last flip-flop


74x597 Parallel Load 8-bit Shift Register IC

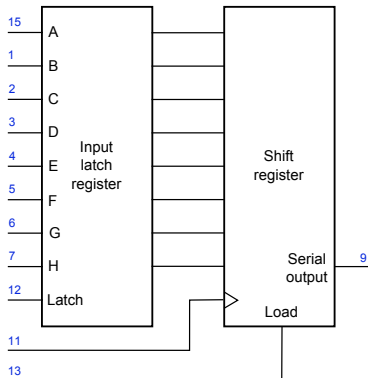Useful for adding input ports to microcontroller with limited pins.



A-H	Data input
Latch	Latch data into input latch register
Load	Transfer data into shift register
Clock	Shift data out
Serial output	Serial data to microcontroller

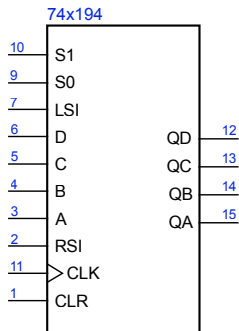74x194 Multi-Function 4-bit Shift Register IC




QD, QC, QB, QA	Parallel data output
D, C, B, A	Parallel data input
LSI	Left shift input
RSI	Right shift input
CLR	Reset all flip-flops
S1, S0	Mode control

S1	S0	Action	QA+	QB+	QC+	QD+
0	0	Hold	QA	QB	QC	QD
0	1	Shift right	RSI	QA	QB	QC
1	0	Shift left	QB	QC	QD	LSI
1	1	Load	A	B	C	D

Ring Counter

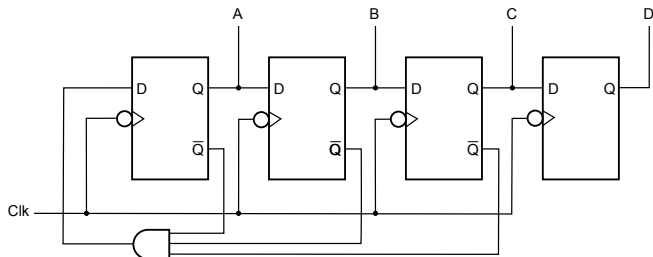
A ring counter is a circular shift register with only one flip-flop being set at any particular time; all others are cleared. The single bit is shifted from one flip-flop to the other to produce the sequence of timing signals.



QA+	QB+	QC+	QD+
1	0	0	0
0	1	0	0
0	0	1	0
0	0	0	1
1	0	0	0

Johnson Counter

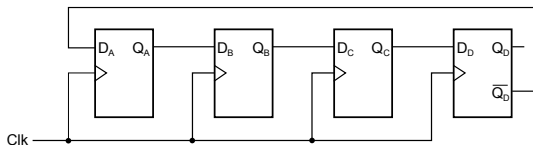
a.k.a. Twisted ring counter, is a variation of the ring counter, with the inverse output of the most significant flip-flop passed to the input of the least significant flip-flop.



QA+	QB+	QC+	QD+
1	0	0	0
1	1	0	0
1	1	1	0
1	1	1	1
0	1	1	1
0	0	1	1
0	0	0	1
0	0	0	0
1	0	0	0

Linear Feedback Shift Register

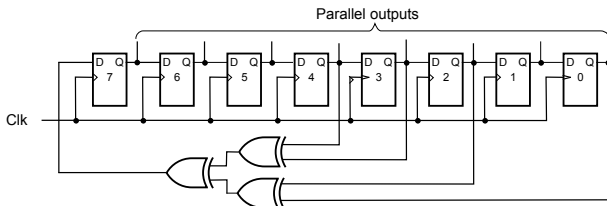A shift register with a pseudo-random output sequence. Period of n -bit LFSR is $2^n - 1$.



Bits	Feedback polynomial
2	$x^2 + x + 1$
3	$x^3 + x^2 + 1$
4	$x^4 + x^3 + 1$
5	$x^5 + x^3 + 1$
6	$x^6 + x^5 + 1$
7	$x^7 + x^6 + 1$
8	$x^8 + x^6 + x^5 + x^4 + 1$