

Chapter 13

Standard Blocks: Counters

SKEE1223 Digital Electronics

Mun'im/Arif/Izam

FKE, Universiti Teknologi Malaysia

December 8, 2015

1 Overview

2 Asynchronous Counters

3 Synchronous Counters

Counter Overview


- A counter is a sequential machine that produces a specified count sequence. The count changes whenever the input clock is asserted.
- Implementation options:
 - **Clock:** Synchronous or Asynchronous
 - **Clock Trigger:** Positive edged or Negative edged
 - **Counts:** Binary, Decade
 - **Count Direction:** Up, Down, or Up/Down
 - **Flip-flops:** JK or T or D
 - **Specialty counters:** Shift register counters, counters with arbitrary sequence

Counters


- **Synchronous counter:**
 - All state bits change synchronously when clock arrives
- **Asynchronous counter:**
 - Changing state bits are used as clocks to subsequent flip-flops → bits do not change at the same time
- For an n -bit counter, the count range is $[0..2^n-1]$

3-bit Up Counter	3-bit Down Counter
000	000
001	111
010	110
011	101
100	100
101	011
110	010
111	001
000	000

A 3-bit Counter


 


State diagram

 


Timing Diagram

Ripple Counters

  


Ripple Counters

 

- Output of any FF goes to clock input of next FF
- Each FF divides input frequency by 2: $f_{in} = 2f_{out}$
- FF outputs change in ripple fashion, not at the same time
- Time for last output to stabilize limits max. counter speed
- Excellent when used as frequency divider
- Note: positive-edge triggered FF counts down

Propagation Delay in Ripple Counters

 



■ Transient states:

- state 111
- state 110 (flip-flop A toggles)
- state 100 (flip-flop B toggles)
- state 000 (flip-flop C toggles)


Max frequency for n -stage ripple counter:

$$f = \frac{1}{T} \leq \frac{1}{nt_p}$$


74x293 Ripple Counter IC

  


74x293 Ripple Counter IC

 

Mod-16 counter.

 


Mod-10 counter.

 


Mod-50 counter.

Synchronous 2-bit Counter

 

Synchronous counter

 


Asynchronous/ripple counter

Characteristics of Synchronous Counters:

- Common clock inputs
- Positive edge triggered FF
- Faster operation


Synchronous 3-bit Counter

 


Mod-8 counter.

- For flip-flop delay t_f and worst case gate delay t_g :
 - Counter propagation delay = $t_f + t_g$
 - Maximum frequency = $\frac{1}{t_f + t_g}$

Synchronous 4-bit Counters

 


4-bit binary (mod-16) counter.

 


Decade (mod-10) counter.

74x163 4-bit Binary Counter IC

 


PE	Parallel load P0-P3 into counter
SR	Synchronous reset
CEP,CET	Count enable
TC	Terminal count (1 means count=1111)

74x163 4-bit Binary Counter IC

 


Mod-13 counter.

 


2..8 counter.

74x163 4-bit Binary Counter IC

 


Mod-256 counter.

74x169 4-bit Binary Up/Down Counter IC

 

PE	Parallel load P0-P3 into counter
U/D*	1 = Count up, 0 = Count down
CEP,CET	Count enable
TC	Terminal count: 0 means count=1111 counting up count=0000 counting down

74x163 as Left/Right Running Light

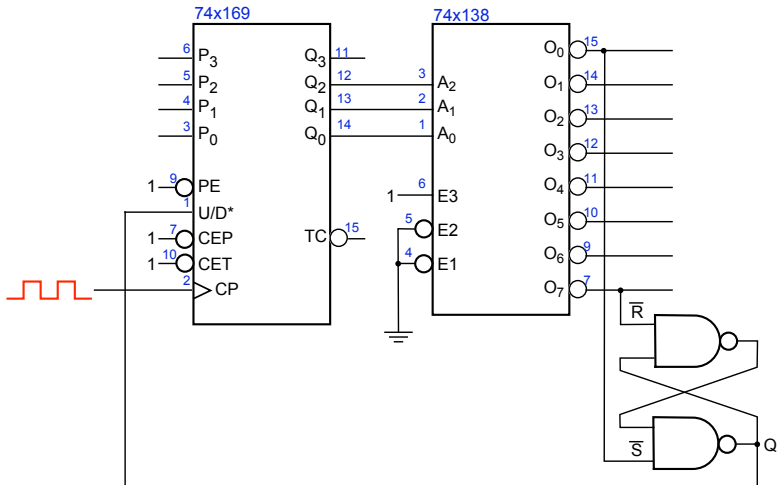



<https://www.openlearning.com/courses/SKEE1223x>