

# Chapter 5

## Arithmetic Circuits

### SKEE2263 Digital Systems


Mun'im Zabidi {munim@utm.my}  
Ismahani Ismail {ismahani@fke.utm.my}  
Izam Kamisian {e-izam@utm.my}

Faculty of Electrical Engineering, Universiti Teknologi Malaysia

March 11, 2018

# Table of Contents

# Iterative Designs

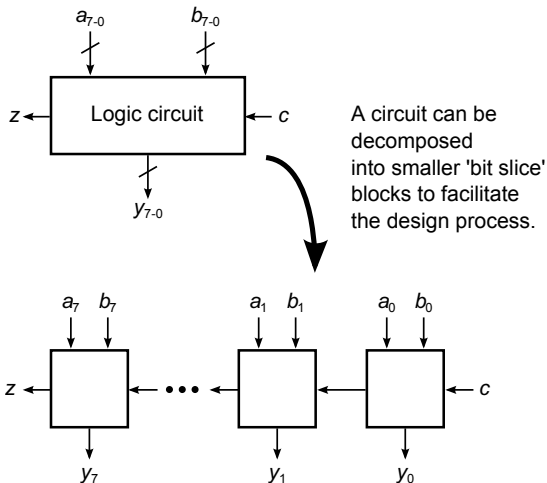


# Half Adder

$a$	$b$	$c$	$s$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$s = a \oplus b$$

$$c = ab$$

 

# Full Adder

## Boolean Expressions


$a_i$	$b_i$	$c_i$	$c_{i+1}$	$s_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$s_i = a_i \oplus b_i \oplus c_i$$

$$c_{i+1} = a_i b_i + a_i c_i + b_i c_i$$


# Full Adder

## Two-Level Realization

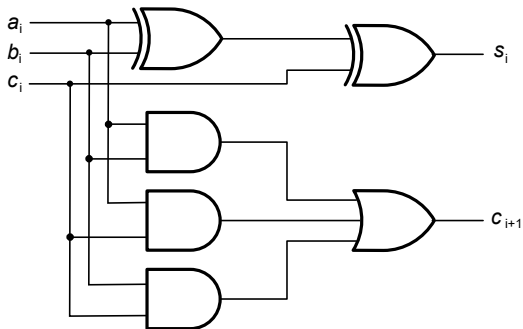

# Full Adder

## Multi-Level, Hierarchical Realization

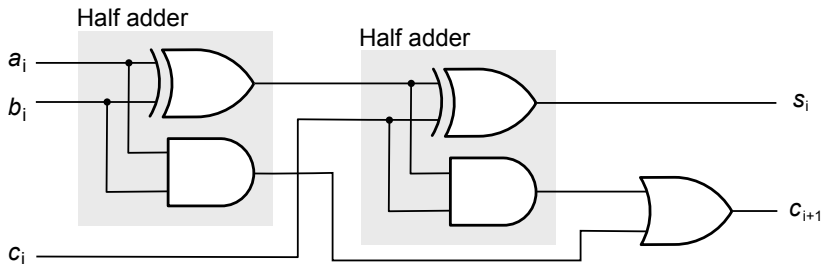

$$s_i = (a_i \oplus b_i) \oplus c_i$$

$$= a_i \oplus b_i \oplus c_i$$



$$c_{i+1} = a_i b_i + (a_i \oplus b_i) c_i$$

$$= a_i b_i + (a_i + b_i) c_i$$

$$= a_i b_i + a_i c_i + b_i c_i$$


# Full Adder

## Schematic for Cascadable Module

 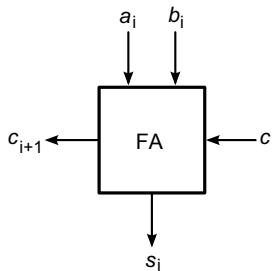





# 4-bit Ripple Adder

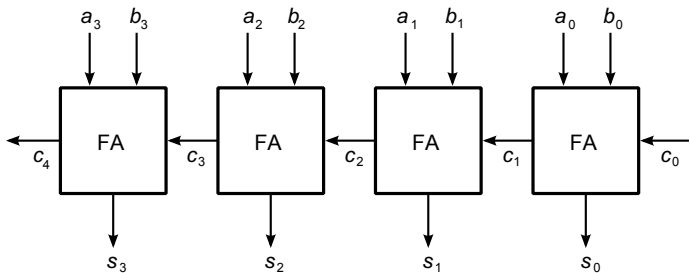

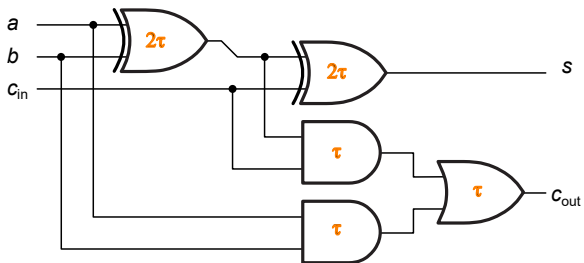
# Delay Analysis of Cascadable Full Adder


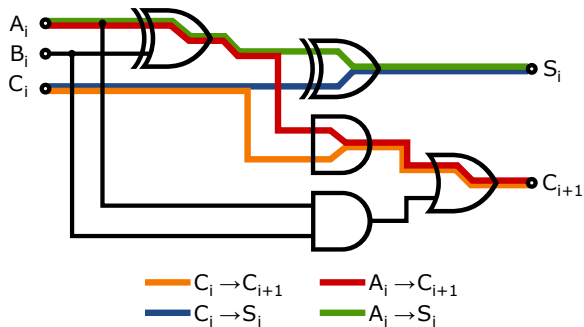
## Delay Analysis of Cascadable Full Adder


 
## Delay Analysis of $n$ -bit Ripple Carry Adder



Delay expression in terms of  $\tau$ :

$$\begin{aligned}t_p &= \text{delay}_{\text{stage } 0} + \text{delay}_{\text{intermediate stages}} + \text{delay}_{\text{stage } n-1} \\ &= 4\tau + [2(n-2)]\tau + 2\tau \\ &= [2n+2]\tau\end{aligned}$$

In “Big(O)”-notation, delay is linear with number of bits

$$O(n)$$

# Carry Lookahead Adder

## Analysis of Carry Behavior

$a_i$	$b_i$	$c_i$	$c_{i+1}$	<b>Decision</b>	$g_i$	$p_i$
0	0	0	0	"Carry kill"	0	0
0	0	1	0		0	0
0	1	0	0	"Carry propagate"	0	1
0	1	1	1		0	1
1	0	0	0		$c_i$	0
1	0	1	1		0	1
1	1	0	1	"Carry generate"	1	1
1	1	1	1		1	1

$c_{i+1} = 1$  :

- when  $a_i = b_i = 1$  (regardless of the carry in) or,
- when  $a_i \neq b_i$  and the carry-in (from the previous stage) is 1

# Carry Lookahead Adder

Derivation of  $p_i, g_i$


- **Carry generate** ( $g_i$ ):  
a signal that is true when  $a_i b_i = 1$ .

$$g_i = a_i b_i$$


- **Carry propagate** ( $p_i$ ):  
propagates the carry-in ( $c_i$ ) to a stage to the next stage (i.e.,  $c_{i+1} \leftarrow c_i$ ) if the “half sum”  $a_i \oplus b_i = 1$ .

$$p_i = a_i + b_i$$

# Carry Lookahead Adder

 

$p_i, g_i$  w.r.t. carries

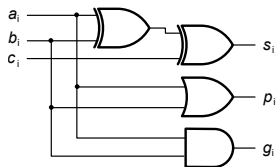

Partial Full Adder (PFA)

# Carry Lookahead Adder

## Carry-out Equations

$$c_1 = g_0 + p_0c_0$$

$$c_2 = g_1 + p_1c_1$$

$$= g_1 + p_1(g_0 + p_0c_0)$$

$$= g_1 + p_1g_0 + p_1p_0c_0$$

$$c_3 = g_2 + p_2c_2$$

$$= g_2 + p_2(g_1 + p_1g_0 + p_1p_0c_0)$$

$$= g_2 + p_2g_1 + p_2p_1g_0 + p_2p_1p_0c_0$$

$$c_4 = g_3 + p_3c_3$$


$$= g_3 + p_3(g_2 + p_2g_1 + p_2p_1g_0 + p_2p_1p_0c_0)$$

$$= g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0 + p_3p_2p_1p_0c_0$$




# Carry Lookahead Adder

## Carry Lookahead Generator (CLG)

 

# Carry Lookahead Adder


## 4-bit Carry Lookahead Adder

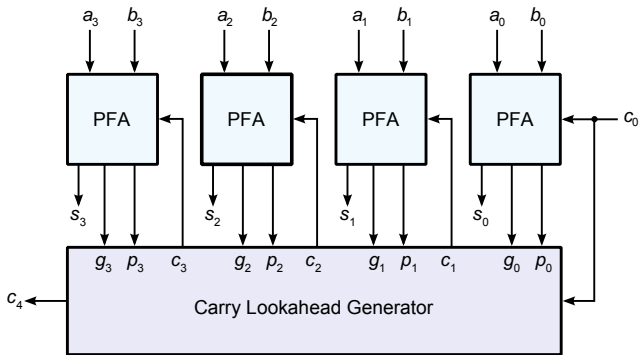

$$\begin{aligned} a_i, b_i &\rightarrow p_i, g_i &= \tau \\ c_0 &\rightarrow c_4 &= 2\tau \\ c_3 &\rightarrow s_3 &= 2\tau \\ \hline \text{Total} & &= 5\tau \end{aligned}$$

# Carry Lookahead Adder
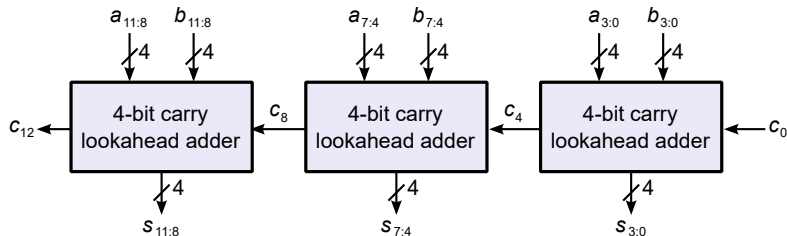
## 12-bit Cascaded Carry Lookahead Adders




$$\begin{aligned} \text{Generate } p_i, g_i \text{ once for whole cascade} &= \tau \\ c_i \rightarrow c_{i+4} \text{ for each block} &= m \times 2\tau \\ c_8 \rightarrow s_{11} &= 2\tau \\ \text{Total} &= [1 + 2m + 2]\tau = [2m + 3]\tau \end{aligned}$$

For 12-bit CLA,  $m = 3$ :

$$[2m + 3]\tau = [2 \times 3 + 3]\tau = 9\tau$$

# Carry Lookahead Adder
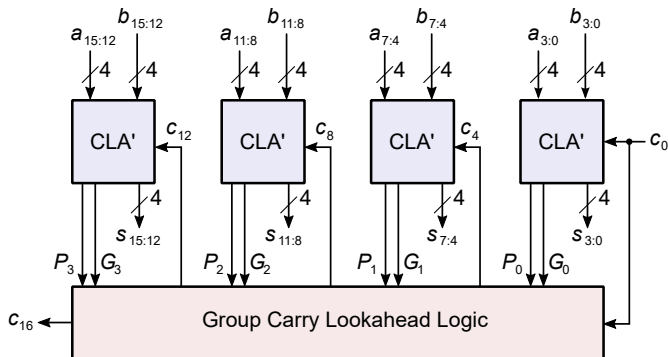
## 16-bit Hierarchical Carry Lookahead Adder



- Total delay =  $8 \tau$ .

# Carry Lookahead Adder

## 16-bit Hierarchical Carry Lookahead Adder

- Group generate

$$G_0 = g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0$$

- Group propagate

$$P_0 = p_3p_2p_1p_0$$

- Interblock carries:

$$c_4 = G_0 + P_0c_0$$

$$c_8 = G_1 + P_1c_4$$

$$= G_1 + P_1G_1 + P_1P_0c_0$$


$$c_{12} = G_2 + P_2c_8$$

$$= G_2 + P_2G_1 + P_2P_1G_1 + P_2P_1P_0c_0$$

$$c_{16} = G_3 + P_3c_{12}$$

$$= G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 + P_3P_2P_1P_0c_0$$


# Carry Select Adder

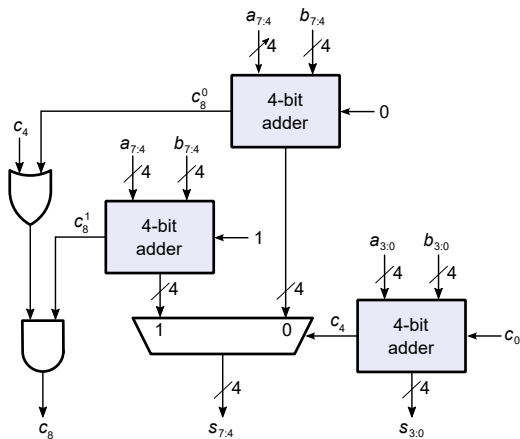

- Total delay = delay of 1 4-bit adder +  $2 \tau$ .

# Carry Save Adder


3:2 Compression Costing Just  $2\tau$

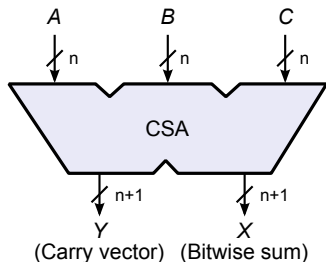

$$\begin{array}{r} A \quad 0 \ 0 \ 1 \ 0 \ 1 \ 1 \\ B \quad 0 \ 1 \ 0 \ 1 \ 0 \ 1 \\ + C \quad 1 \ 1 \ 1 \ 1 \ 0 \ 1 \\ \hline S \quad 0 \ 1 \ 0 \ 0 \ 0 \ 1 \ 1 \\ C \quad 0 \ 1 \ 1 \ 1 \ 0 \ 1 \ 0 \\ \hline \Sigma \quad 1 \ 0 \ 1 \ 1 \ 1 \ 0 \ 1 \end{array}$$
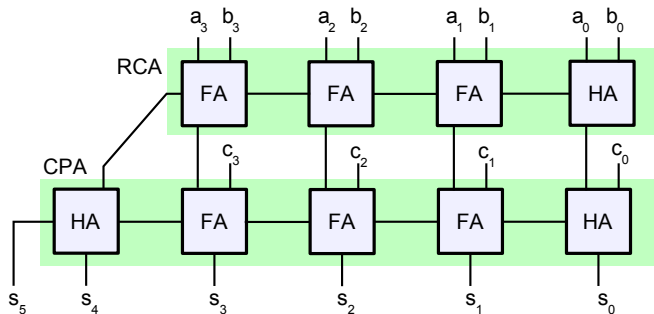
# Carry Save Adder

Adding 3 numbers using Ripple Carry Adders only




Delay  $14\tau$




# Carry Save Adder

Adding 3 numbers using Carry Save Adders

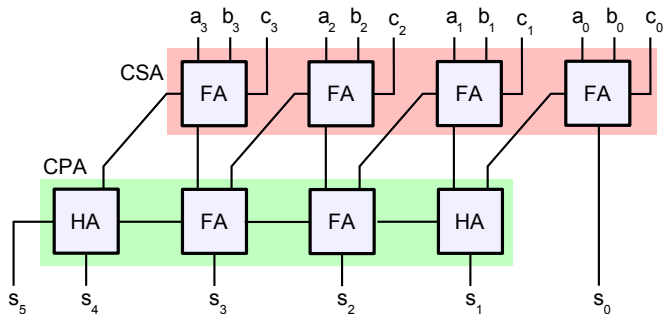

Delay  $12\tau$

# Adder Delay Summary

 


# Half Subtractor

Input		Output	
<i>a</i>	<i>b</i>	<i>r</i> (borrow)	<i>d</i> (difference)
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

$$d = a'b + ab'$$

$$= a \oplus b$$

$$r = a'b$$

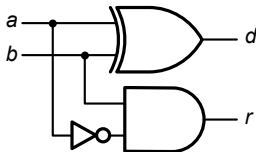

# Full Subtractor

Input			Output	
$a$	$b$	$r_i$	$r_{i+1}$	$d$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


$$d = a'b'r_i + a'br'_i + ab'r'_i + abr_i$$

$$= a \oplus b \oplus r_i$$


$$r_{i+1} = a'b'r_i + a'br'_i + a'br_i + abr_i$$

$$= a'r_i + a'b + br_i$$


# Full Subtractor

 

# Ripple Subtractor

 

# Subtraction by Adding

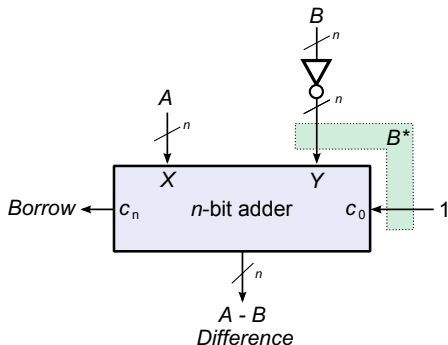


$$\begin{aligned} S &= A + \overline{B} + 1 \\ &= A + B^* \\ &= A + (2^n - B) \\ &= A - B + 2^n \\ &= A - B \end{aligned}$$

where:

- $\overline{B}$ : Ones' complement of  $B$
- $B^*$ : Two's complement of  $B$

# Adder/Subtractor

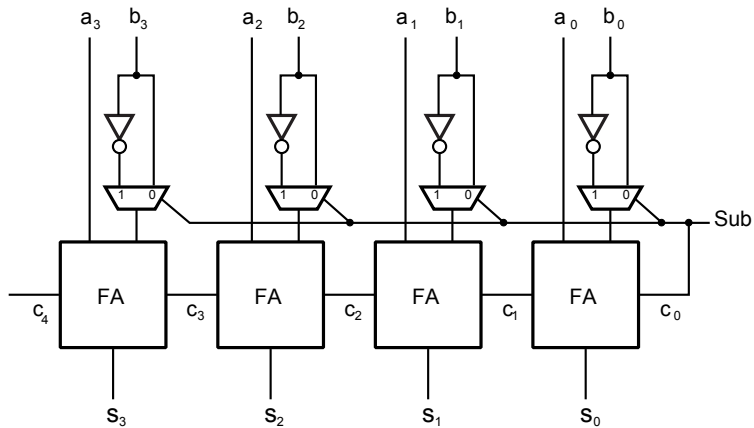



# Flags

<b>Code</b>	<b>Name</b>	<b>Significance</b>
Z	Zero	Result is zero
N	Negative	Result is $< 0$
C	Carry	The most significant bit produced a carry
V	Overflow	Result has too many bits to be represented correctly

## Z Flag

True when all the bits in an  $n$ -bit result are 0s.

$$\begin{aligned} Z &= s'_{n-1} s'_{n-2} \cdots s'_1 s'_0 \\ &= (s_{n-1} + s_{n-2} + \cdots + s_1 + s_0)' \end{aligned}$$

## N Flag

The negative flag (N) is simply the sign bit. When it is high, the result was less than zero.

$$N = s_{n-1}$$

# C Flag

The carry out from the adder

$$C = c_n$$

## V Flag

True when a calculation produces a result that is greater than a register can store

$a_{n-1}$	$b_{n-1}$	$s_{n-1}$	$c_{n-1}$	$c_{n-2}$	$V$
0	0	0	0	0	0
0	0	1	0	1	1
1	1	0	1	0	1
1	1	1	1	1	0


Method 1:

$$V = a_{n-1}b_{n-1}s'_{n-1} + a'_{n-1}b'_{n-1}s_{n-1}$$

Method 2:

$$V = c_n \oplus c_{n-1}$$

# Flags Circuit

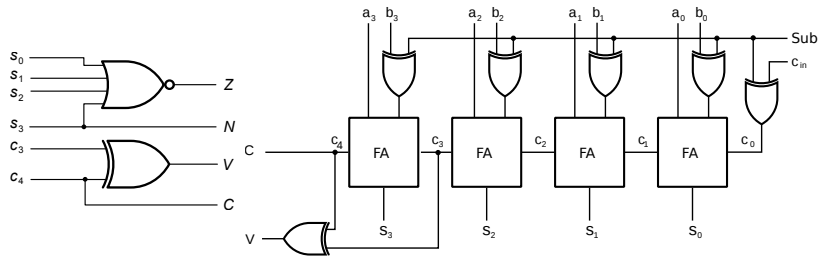

## Deriving Other Relations

Math Symbol	Description	Flags (Unsigned)	Flags (Signed)
=	Equal		Z
≠	Not equal		Z'
<	Less than	C'	$N \oplus V$
≤	Less than or equal	$C' + Z$	$Z + (N \oplus V)$
≥	Greater than or equal	C	$N \odot V$
>	Greater than	$C \cdot Z'$	$Z' \cdot (N \odot V)$

# Binary Multiplication

$$\begin{array}{r} \phantom{\times} 1\ 1\ 0\ 1 \\ \times 1\ 0\ 1\ 1 \\ \hline \phantom{\times} 1\ 1\ 0\ 1 \\ \phantom{\times} 1\ 1\ 0\ 1 \\ \phantom{\times} 0\ 0\ 0\ 0 \\ \phantom{\times} 1\ 1\ 0\ 1 \\ \hline 1\ 0\ 0\ 0\ 1\ 1\ 1\ 1 \end{array}$$

$(13)_{10}$     Multiplicand  $M$   
 $(11)_{10}$     Multiplier  $Q$

} Partial Products

$(143)_{10}$     Product  $P$


Multiplication is all about:

- 1 Generating the partial products
- 2 Adding the partial products



 
## 2 × 2 Multiplication


$$\begin{array}{r} \times \quad a_1 \quad a_0 \\ \quad b_1 \quad b_0 \\ \hline a_1 b_1 \quad a_0 b_1 \\ a_1 b_0 \quad a_0 b_0 \\ \hline p_3 \quad p_2 \quad p_1 \quad p_0 \end{array}$$



# Ripple Carry Array Multiplier

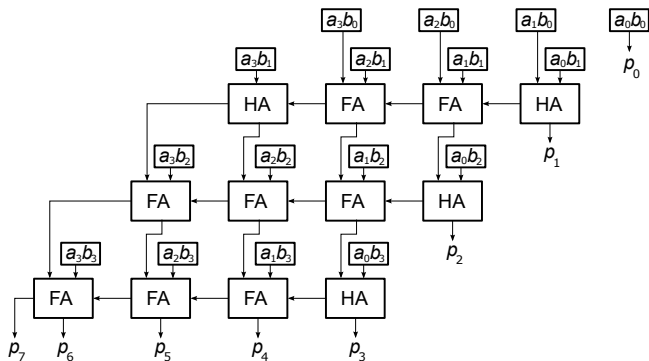

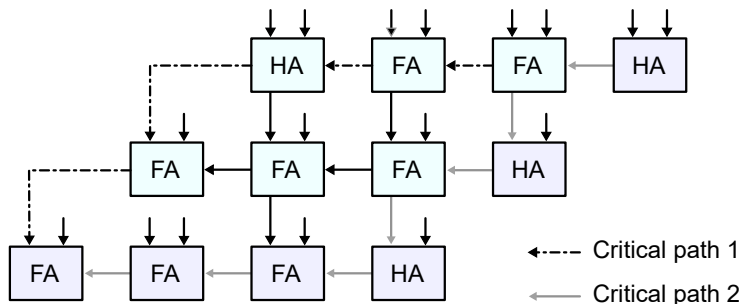
## $M \times N$ Array Multiplier Critical Paths




Source: <http://www.slideshare.net/ankitgoel/cmos-arithmetic-circuits>

# Carry Save Adder Multiplier

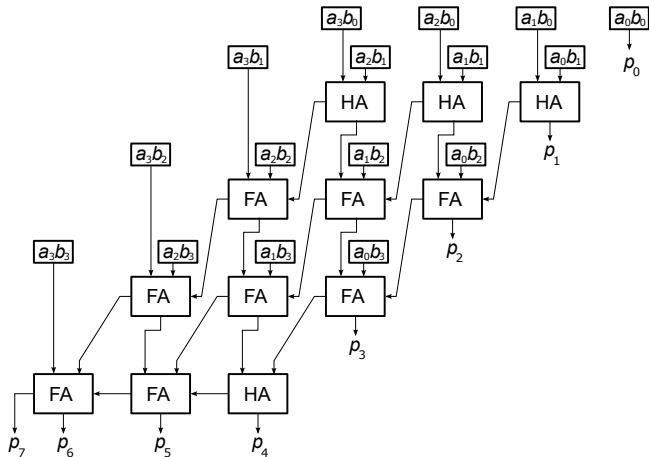

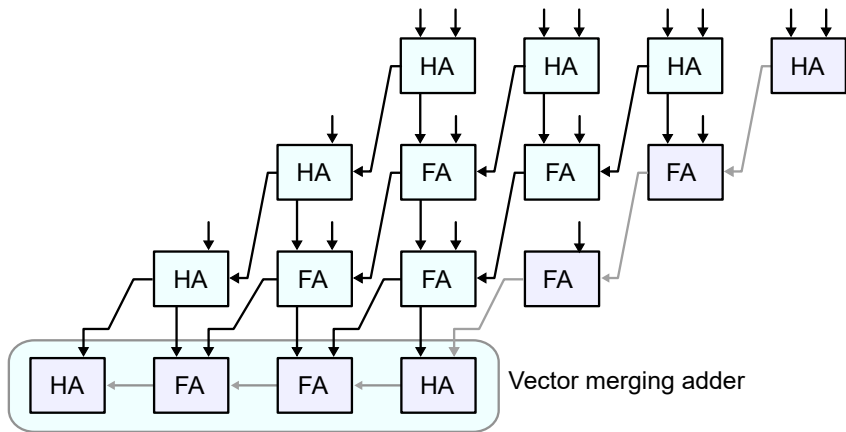
# Carry Save Adder Multiplier Critical Path



Source: <http://www.slideshare.net/ankitgoel/cmos-arithmetic-circuits>



# Wallace Tree Multiplier

An application of carry save adder

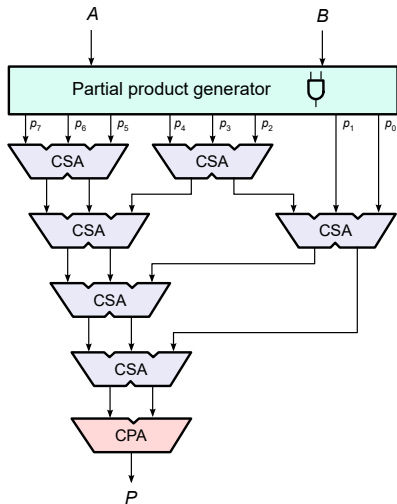

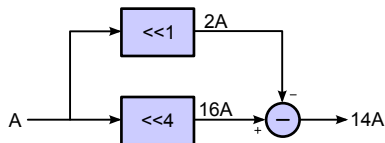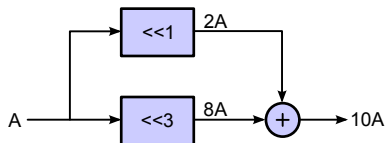
## Multiplication with Constants

- Constants with long strings of 0s or 1s can be multiplied very efficiently using just a few adders.
- Remember that shifting a number one bit = multiplication by 2



# Lookup Table (LUT) Multipliers

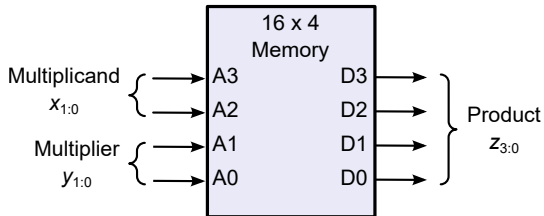

$A_3 A_2$	$A_1 A_0$			
	00	01	10	11
00	0000	0000	0000	0000
01	0000	0001	0010	0011
10	0000	0010	0100	0110
11	0000	0011	0110	1001