

# Chapter 7

## Sequential Logic

### SKEE2263 Digital Systems

Mun'im Zabidi {munim@utm.my}  
Ismahani Ismail {ismahani@fke.utm.my}  
Izam Kamisian {e-izam@utm.my}

Faculty of Electrical Engineering, Universiti Teknologi Malaysia

February 10, 2018

# Table of Contents


**1** Intro

**2** Bistable Circuits

**3** FF Characteristics

**4** FF Excitation

# Classes of Digital Circuits

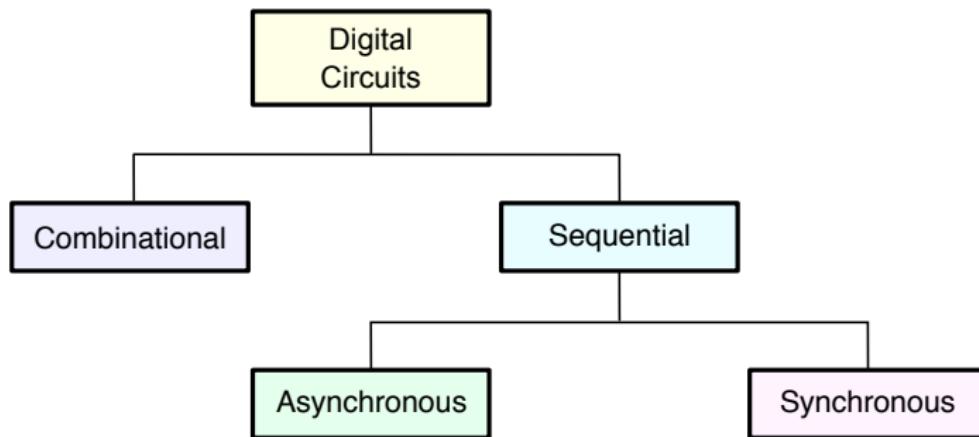

# Sequential vs Combinational

## ■ Combinational:



- Output =  $f(\text{Present Input})$
- Memoryless

## ■ Sequential:


- Output =  $f(\text{Present Input}, \text{Past Input})$
- Uses latches/flip-flop as memory
- May have clock input (synchronous) or not (asynchronous)
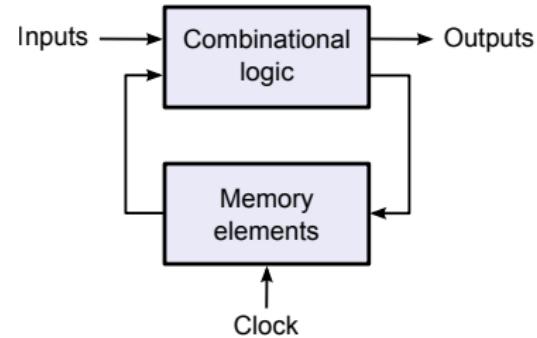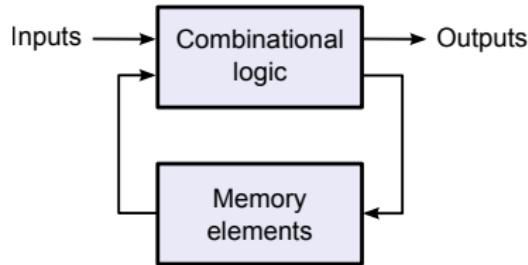
# Clocks

- Asynchronous sequential circuits have no clock input




# Clock Parts

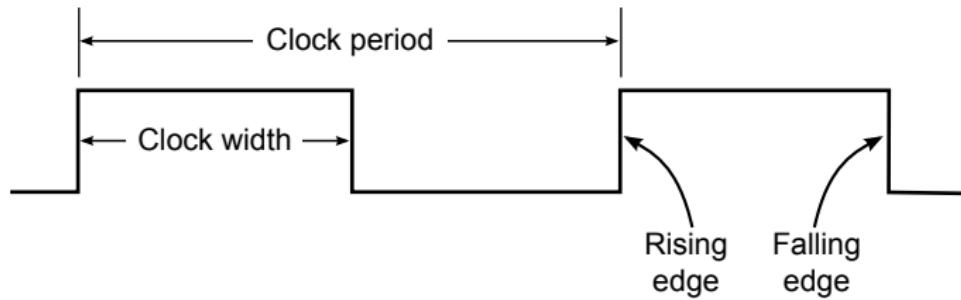

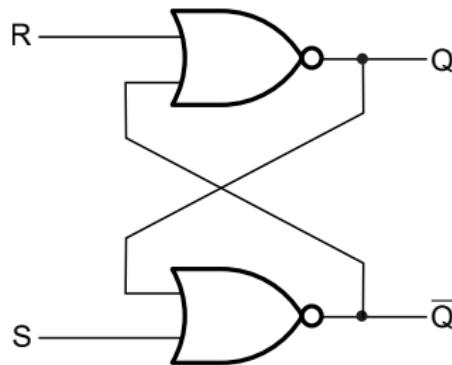
# SR Latch: Gate Level

- Bistable circuits: stable in state 0 or 1
- Simplest bistable is SR latch



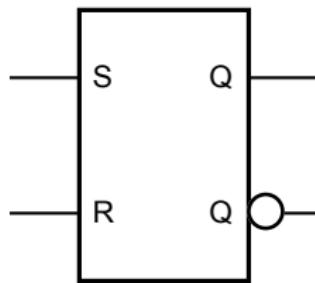
# SR Latch: Logic Symbol, Characteristic Table




| S | R | $Q^+$ | $\bar{Q}^+$ | Action    |
|---|---|-------|-------------|-----------|
| 0 | 0 | Q     | $\bar{Q}$   | No change |
| 0 | 1 | 0     | 1           | Reset     |
| 1 | 0 | 1     | 0           | Set       |
| 1 | 1 | 0     | 0           | Forbidden |

# SR Latch: Timing Diagram

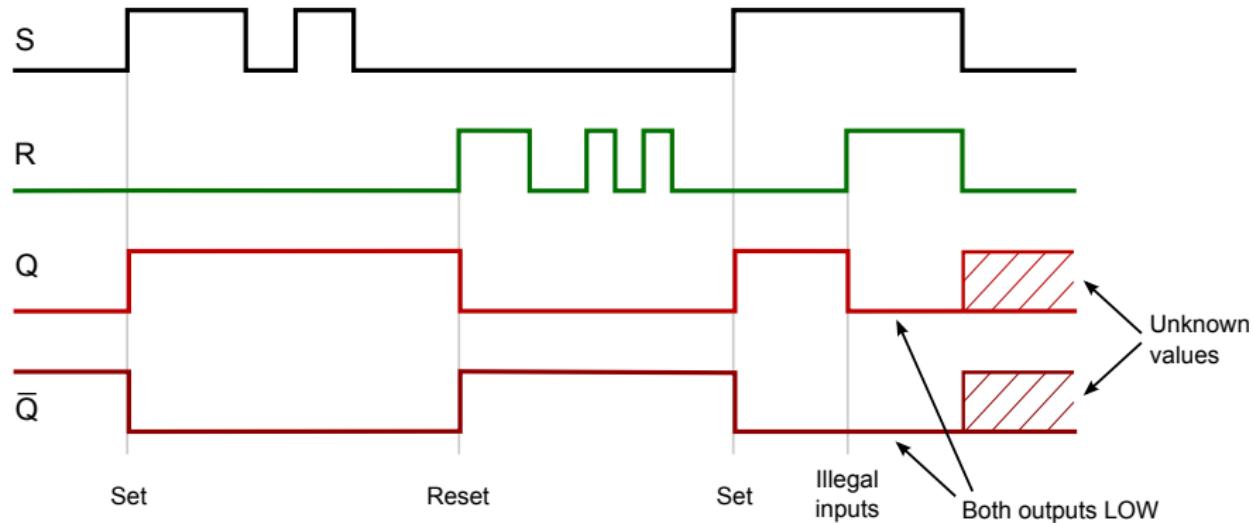

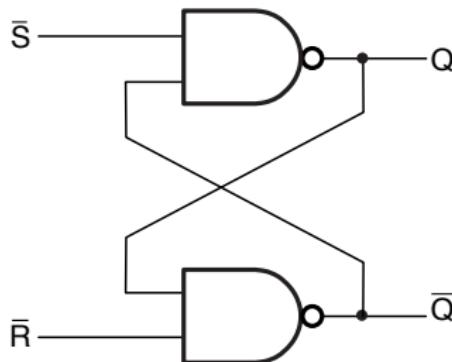
# $\overline{S} \overline{R}$ Latch: Gate Level, Characteristic Table




| S | R | $Q^+$ | $\bar{Q}^+$ | Action    |
|---|---|-------|-------------|-----------|
| 0 | 0 | 1     | 1           | Forbidden |
| 0 | 1 | 1     | 0           | Set       |
| 1 | 0 | 0     | 1           | Reset     |
| 1 | 1 | Q     | $\bar{Q}$   | No change |
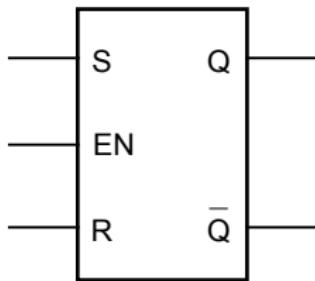
# Gated SR Latch: Logic Symbol, Characteristic Table




| EN | S | R | $Q^+$ | Action    |
|----|---|---|-------|-----------|
| 0  | x | x | Q     | No change |
| 1  | 0 | 0 | Q     | No change |
| 1  | 0 | 1 | 0     | Reset     |
| 1  | 1 | 0 | 1     | Set       |
| 1  | 1 | 1 | x     | Forbidden |

# Gated SR Latch: Timing Diagram

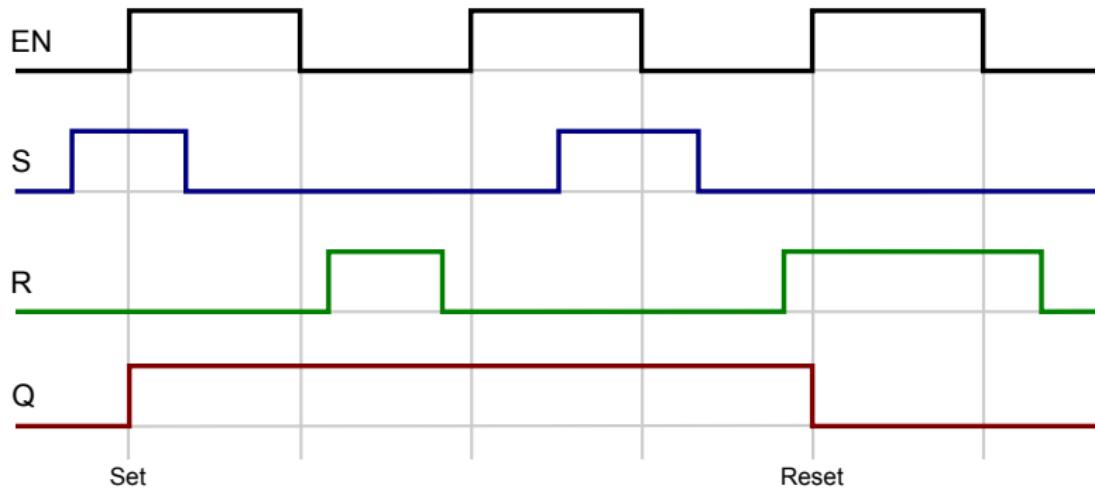

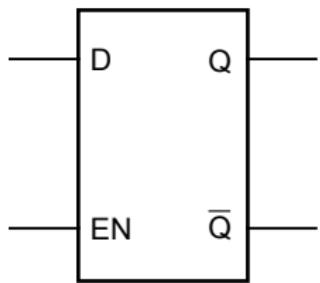
# Gated D Latch: Logic Symbol, Characteristic Table




| EN | D | $Q^+$ | Action           |
|----|---|-------|------------------|
| 0  | x | Q     | Storage state    |
| 1  | 0 | 0     | Transparent mode |
| 1  | 1 | 1     | Transparent mode |

# Gated D Latch: Timing Diagram


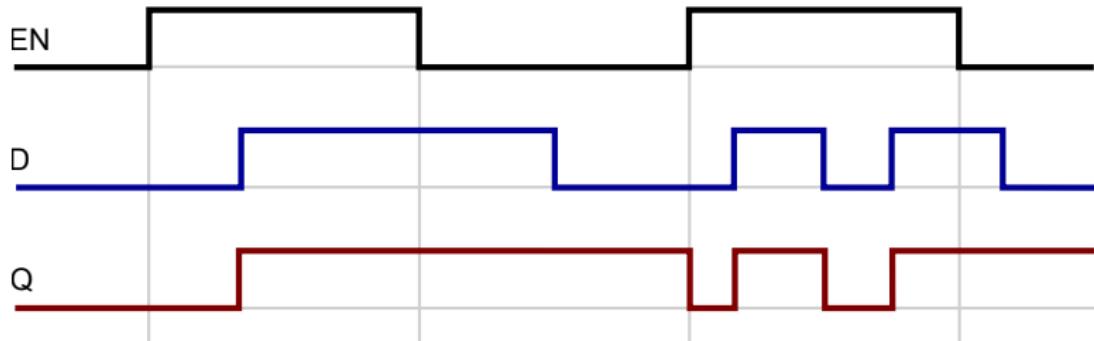

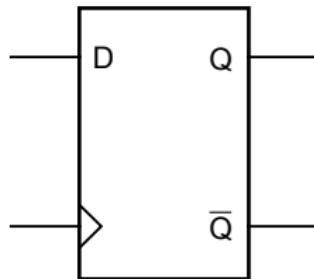
# D Flip-Flop: Logic Symbol, Characteristic Table




| Clock | D | $Q^+$ | Action    |
|-------|---|-------|-----------|
| 0     | x | Q     | No change |
| 1     | x | Q     | No change |
| ↑     | 0 | 0     | Reset     |
| ↑     | 1 | 1     | Set       |

# D Flip-Flop vs Latch

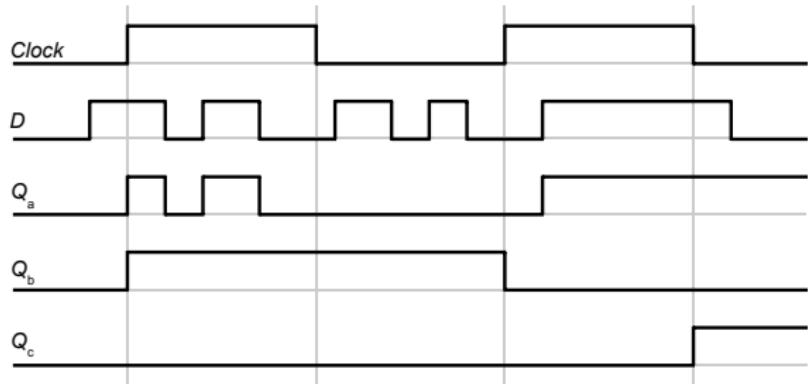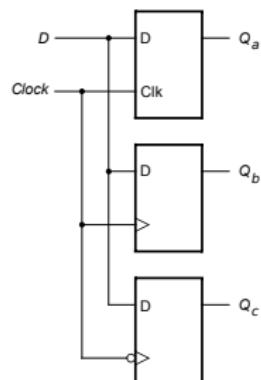

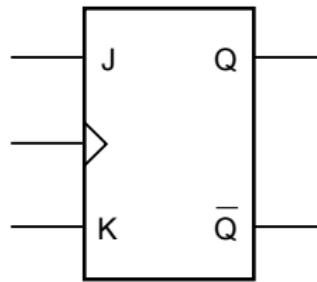
# JK Flip-Flop: Logic Symbol, Characteristic Table




| Clk | J | K | $Q^+$ | Action    |
|-----|---|---|-------|-----------|
| 0   | x | x | Q     | No change |
| 1   | x | x | Q     | No change |
| ↑   | 0 | 0 | Q     | No change |
| ↑   | 0 | 1 | 0     | Reset     |
| ↑   | 1 | 0 | 1     | Set       |
| ↑   | 1 | 1 | $Q'$  | Toggle    |
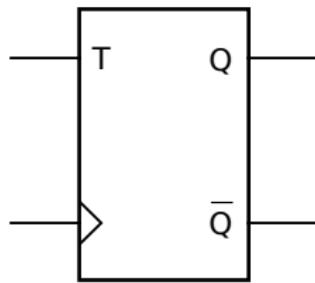
# T Flip-Flop: Logic Symbol, Characteristic Table



| Clk | T | $Q^+$     | Action    |
|-----|---|-----------|-----------|
| 0   | × | Q         | No change |
| 1   | × | Q         | No change |
| ↑   | 0 | Q         | No change |
| ↑   | 1 | $\bar{Q}$ | Toggle    |

# FF Timing Parameters

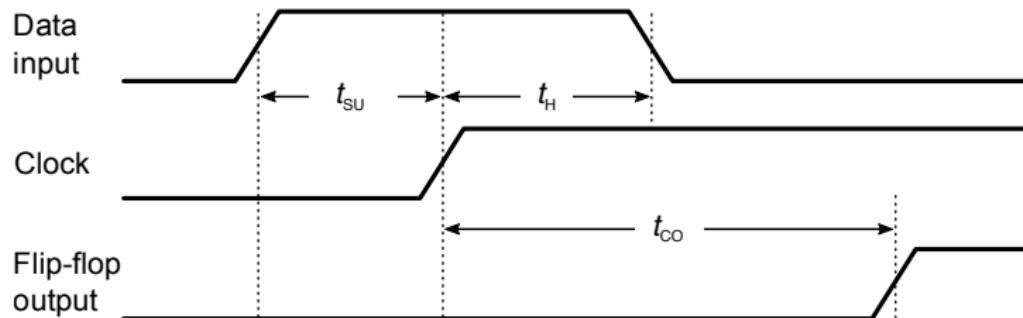


# FF Timing Parameters

**Setup time,  $t_{SU}$**  – the minimum time that a flip-flop input must be stable before the clock edge.

**Hold time,  $t_H$**  – the minimum time after the clock edge that a flip-flop input must continue to be in the same stable state.

**Clock to output delay time,  $t_{CO}$**  – the minimum time after a clock edge to obtain a valid output


# Setup Time Violation

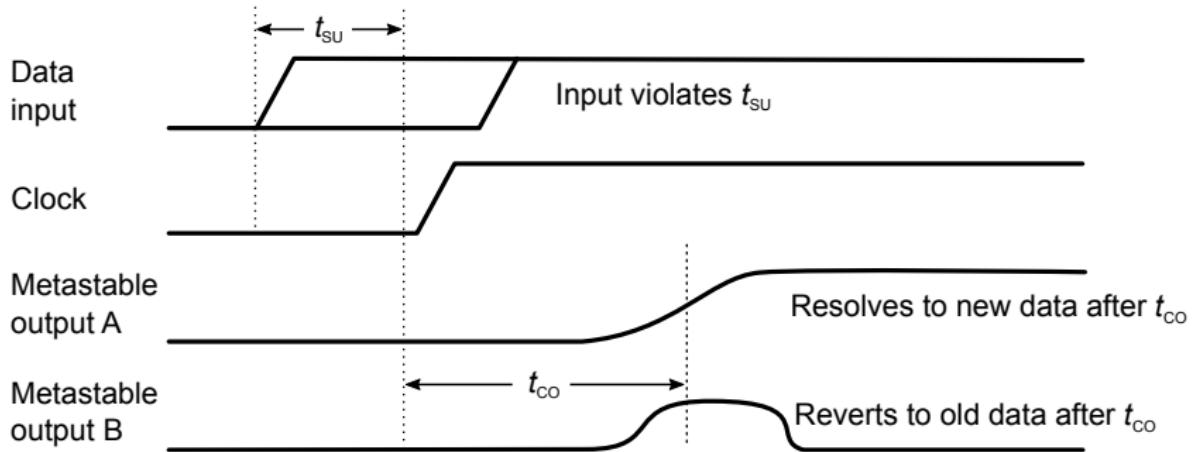

# Causes of Metastability




Asynchronous Inputs.

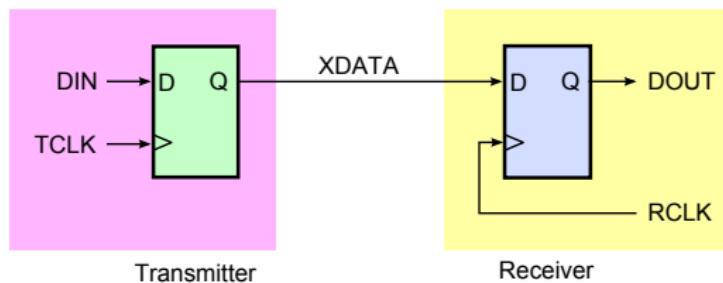


Data transfer across clock domains.

# What Happens During Metastability

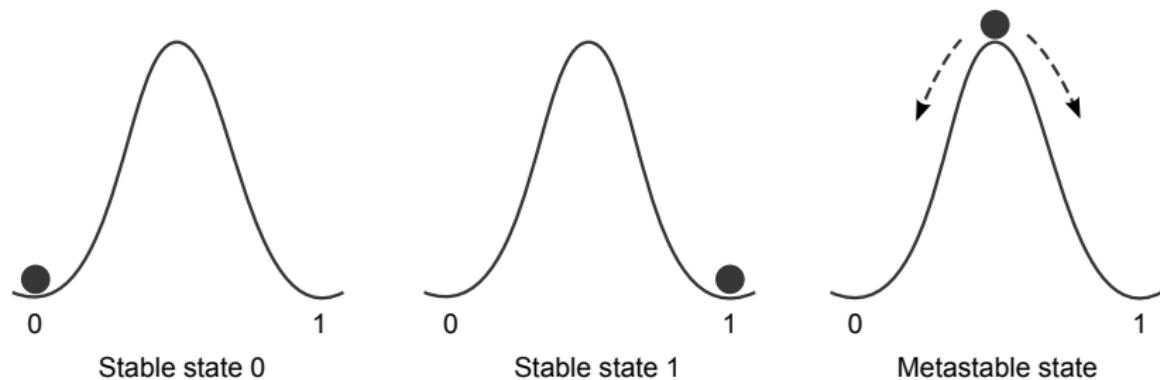

# Solution for Metastability

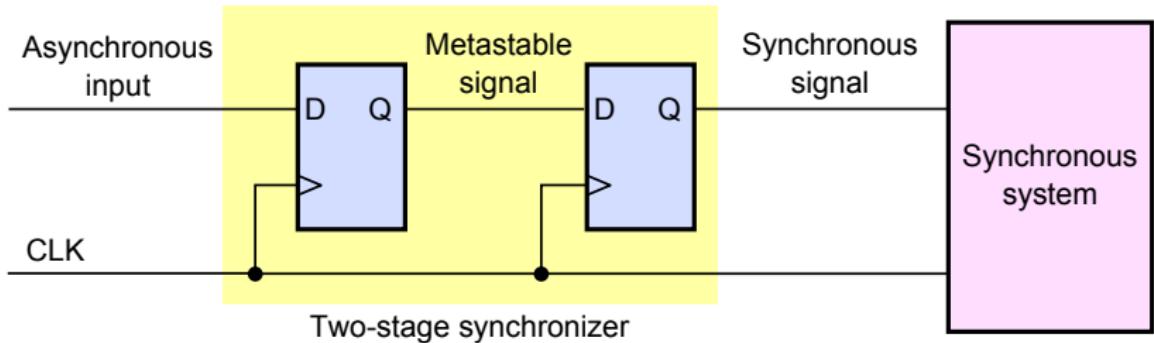

# D Flip-Flop


**Characteristic table:**

| D | $Q^+$ | Operation |
|---|-------|-----------|
| 0 | 0     | Reset     |
| 1 | 1     | Set       |

**Excitation table:**

| Present State<br>Q | Next State<br>$Q^+$ | Input<br>D |
|--------------------|---------------------|------------|
| 0                  | 0                   | 0          |
| 0                  | 1                   | 1          |
| 1                  | 0                   | 0          |
| 1                  | 1                   | 1          |

**State diagram:**

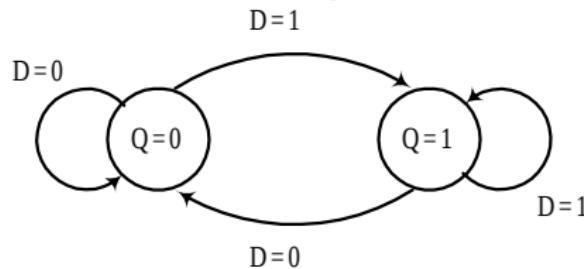

**Characteristic Equation:**

$$Q^+ = D$$

# T Flip-Flop


**Characteristic table:**

| T | $Q^+$ | Operation  |
|---|-------|------------|
| 0 | Q     | No change  |
| 1 | $Q'$  | Complement |

**Excitation table:**

| Present State<br>Q | Next State<br>$Q^+$ | Input<br>T |
|--------------------|---------------------|------------|
| 0                  | 0                   | 0          |
| 0                  | 1                   | 1          |
| 1                  | 0                   | 1          |
| 1                  | 1                   | 0          |

**State diagram:**

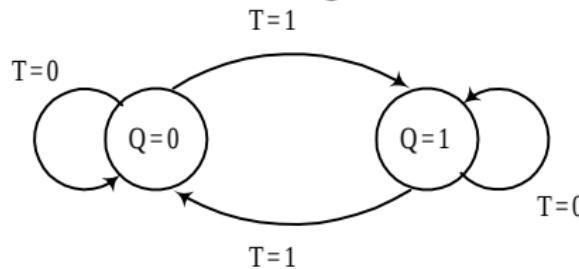

**Characteristic Equation:**

$$Q^+ = T'Q + TQ' = T \oplus Q$$

# JK Flip-Flop

**Characteristic table:**

| J | K | $Q^+$ | Operation  |
|---|---|-------|------------|
| 0 | 0 | Q     | No change  |
| 0 | 1 | 0     | Reset      |
| 1 | 0 | 1     | Set        |
| 1 | 1 | $Q'$  | Complement |

**Excitation table:**


| Present State<br>Q | Next State<br>$Q^+$ | Inputs |   |
|--------------------|---------------------|--------|---|
|                    |                     | J      | K |
| 0                  | 0                   | 0      | x |
| 0                  | 1                   | 1      | x |
| 1                  | 0                   | x      | 1 |
| 1                  | 1                   | x      | 0 |

**State diagram:**

JK=10 or 11

**Characteristic Equation:**

$$Q^+ = J\bar{Q} + \bar{K}Q$$

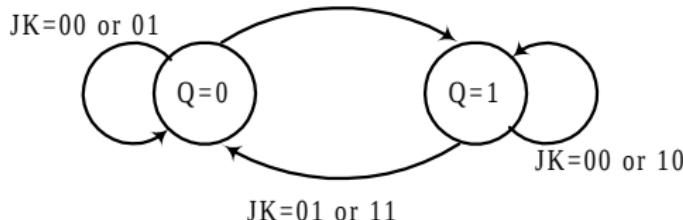

# SR Flip-Flop

**Characteristic table:**


| S | R | $Q^+$ | Operation |
|---|---|-------|-----------|
| 0 | 0 | Q     | No change |
| 0 | 1 | 0     | Reset     |
| 1 | 0 | 1     | Set       |
| 1 | 1 | ?     | Undefined |

**Excitation table:**

| Present State<br>Q | Next State<br>$Q^+$ | Inputs |   |
|--------------------|---------------------|--------|---|
|                    |                     | S      | R |
| 0                  | 0                   | 0      | x |
| 0                  | 1                   | 1      | 0 |
| 1                  | 0                   | 0      | 1 |
| 1                  | 1                   | x      | 0 |

**State diagram:**

SR=10

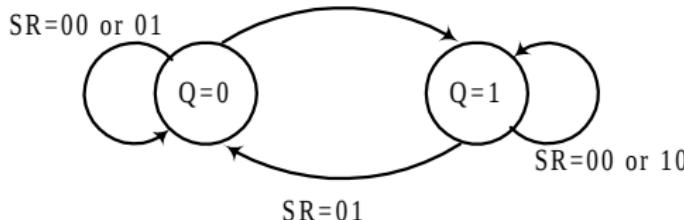

**Characteristic Equation:**

$$Q^+ = S + \overline{R}Q$$

$$SR \neq 1$$

# Excitation Table Summary

| <b>Q</b> | <b>Q<sup>+</sup></b> | <b>S</b> | <b>R</b> | <b>D</b> | <b>J</b> | <b>K</b> | <b>T</b> |
|----------|----------------------|----------|----------|----------|----------|----------|----------|
| 0        | 0                    | 0        | ×        | 0        | 0        | ×        | 0        |
| 0        | 1                    | 1        | 0        | 1        | 1        | ×        | 1        |
| 1        | 0                    | 0        | 1        | 0        | ×        | 1        | 1        |
| 1        | 1                    | ×        | 0        | 1        | ×        | 0        | 0        |