

Chapter 8

Registers

SKEE2263 Digital Systems

Mun'im Zabidi {munim@utm.my}
Ismahani Ismail {ismahani@fke.utm.my}
Izam Kamisian {e-izam@utm.my}


Faculty of Electrical Engineering, Universiti Teknologi Malaysia

September 22, 2018



Table of Contents

- 1 Registers
- 2 Shift Registers
- 3 Accumulators
- 4 Register Files
- 5 Register Transfer Language



Basic Register

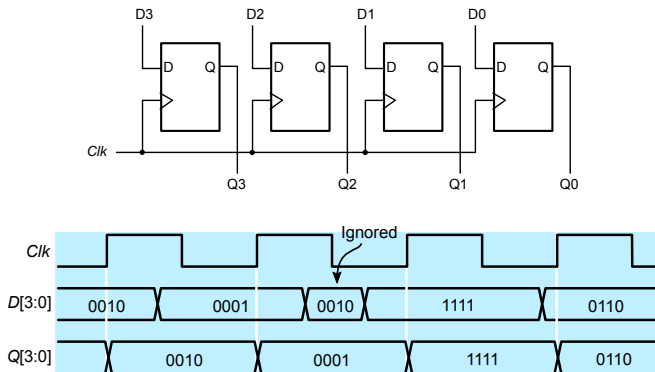


Resettable Register

  


Register with Load Enable

  


Basic Shift Register

 



Shift Register “Animation”

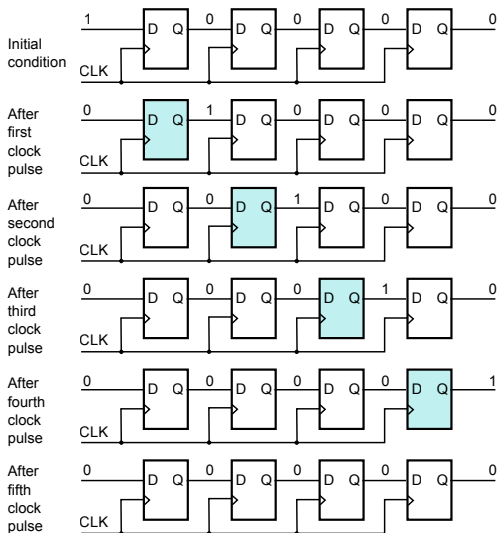


Shift Register Timing Diagram

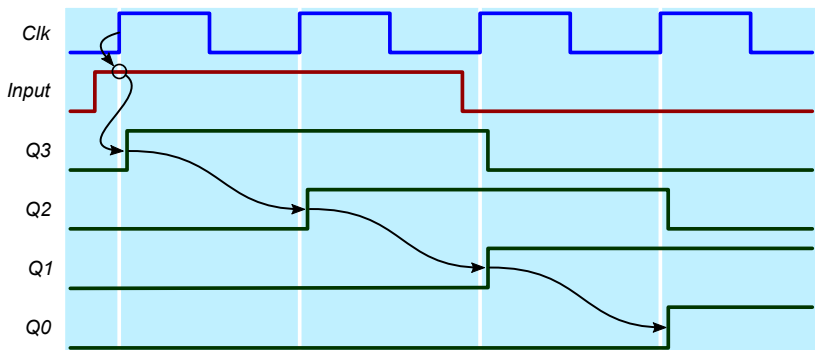

Enabled Shift Register

  


Universal Shift Register

 


S_1	S_0	Function
0	0	Hold
0	1	Shift left
1	0	Shift right
1	1	Load new input

- Can be used in either serial-to-serial, serial-to-parallel, parallel-to-serial, parallel-to-parallel, left shifting as well as right shifting.
- Useful in arithmetic operations to shift data left for multiplication or to shift data right for division.


Universal Shift Register Schematic

 


Universal Shift Register Timing Diagram

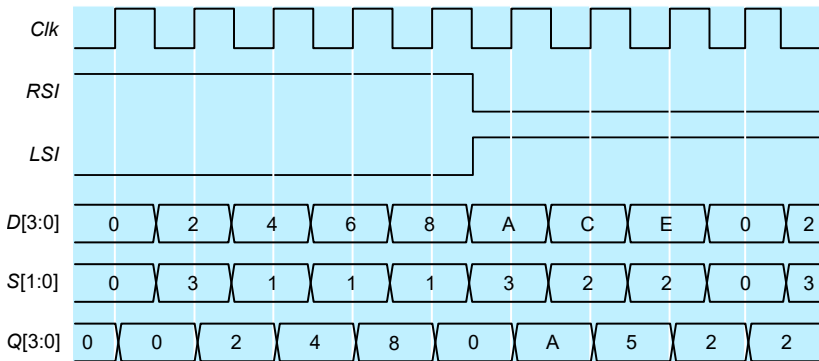


Accumulators

 

 
- Accumulator: register that keeps results of arithmetic ops.
- Registers + Adders \rightarrow Accumulator-based counter.
- Any adder architecture may be used.



6-bit Accumulator-Based Counter

 

Resettable Counter

 


Clear	Function
0	Run
1	Clear

Check your understanding.


This is Milestone 2.

Multi-Function Counter No.1

 


S1	S0	Function
0	0	Clear
0	1	Add 1
1	0	Add 2
1	1	Subtract 1

Multi-Function Counter No.2


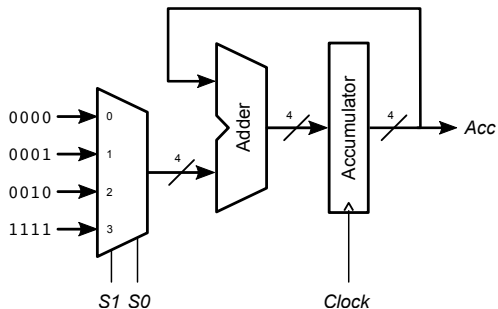


S1	S0	Function
0	0	Hold
0	1	Add 1
1	0	Add 2
1	1	Subtract 1


Prescaler

 

Timer

  


Timer

 

Register Files vs RAM

	Register Files	RAM
Capacity	Small	Large
Speed	Fast	Slow
Ease of Design	Easy	Harder


Minimal Register File

 


Four 8-bit registers

- DataIn : n -bit input
- DataOut : n -bit output
- WriteAddr: $\log_2 n$ -bit write address
- ReadAddr: $\log_2 n$ -bit read address
- WriteEn: write enable

Minimal Register File

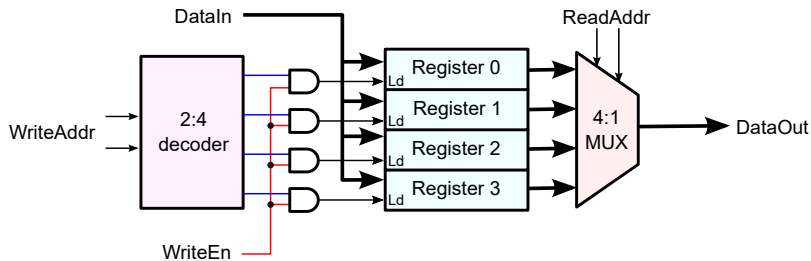

Register File with 2 Read Ports

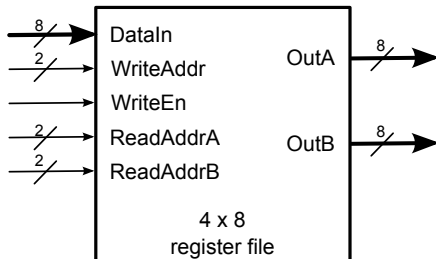

Register File with 2 Read Ports

