

Chapter 10

Finite State Machine Synthesis

SKEE2263 Digital Systems

Mun'im Zabidi {munim@utm.my}
Ismahani Ismail {ismahani@fke.utm.my}
Izam Kamisian {e-izam@utm.my}

Faculty of Electrical Engineering, Universiti Teknologi Malaysia

February 10, 2018

Table of Contents

- 1 Design Process
- 2 Single-Mode Counters
- 3 Multimode Counters
- 4 Sequence Detectors
 - 110 Sequence Detector
 - Alternating Input Detector

FSM Design Process

Step	Description
<i>Conceptualize</i>	Understand the statement of the specification.
<i>Capture the FSM</i>	Translate the problem into state diagram. Determine the number of states required, inputs , outputs and state transitions .
<i>Encode the states</i>	Assign a unique binary number to each state.
<i>Create the state table</i>	Create a truth table for the combinational logic for next state generation and output decoding.
<i>Extract the equations</i>	Express the logic circuits as Boolean equations.
<i>Implement the FSM</i>	Enter and verify the design.

Counters


- Definition of counters:
 - Starts from a particular state
 - Goes thru fixed sequence of states
 - Returns to initial state
 - Repeats indefinitely
- Most counters (but not all) are Medvedev state machines
 - Medvedev machine have not output logic.
 - Register outputs = system outputs.
- Single-mode counters:
 - The only input is the clock signal
- Multi-mode counters:
 - Has input to select mode of operation

2-bit Binary Counter

Binary Counters

n state variables $\Rightarrow 2^n$ sequential states

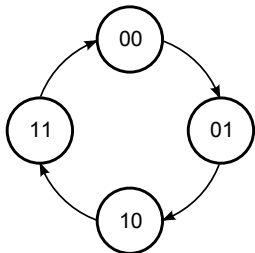Binary 2-bit counter : straight binary sequence $0 \rightarrow 1 \rightarrow 2 \rightarrow 3 \rightarrow 0$




Present State		Next State	
Q_1	Q_0	Q_1^+	Q_0^+
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

2-bit Binary Counter

Present State		Next State	
Q_1	Q_0	Q_1^+	Q_0^+
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0


$$Q_1^+ = Q_1 \oplus Q_0$$

$$Q_0^+ = Q_0'$$

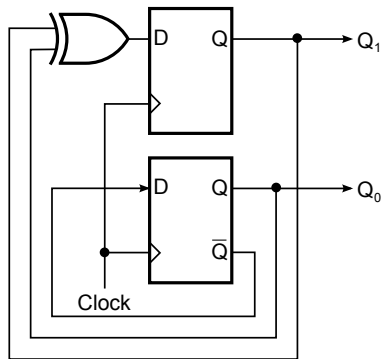

Counter with Arbitrary Sequence

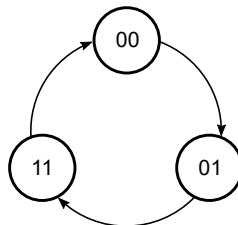- Counter next states can be non-sequential
- Number of states can be $< 2^n$
- All valid:
 - $0 \rightarrow 3 \rightarrow 1 \rightarrow 2 \rightarrow 0$,
 - $0 \rightarrow 1 \rightarrow 3 \rightarrow 2 \rightarrow 0$,
 - $0 \rightarrow 1 \rightarrow 3 \rightarrow 0$




Counter with Arbitrary Sequence

Present State		Next State	
Q_1	Q_0	Q_1^+	Q_0^+
0	0	0	1
0	1	1	1
1	0	×	×
1	1	0	0

$$Q_1^+ = Q_1' Q_0$$

$$Q_0^+ = Q_1'$$

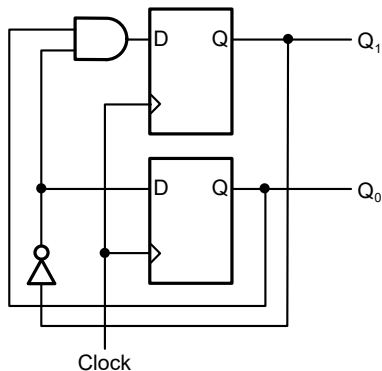

Definition


Multi-Mode Counter

A counter whose counting sequence depends not only on the clock but also on some other control signal(s).

Examples:

- Counts up or down
- Counts in binary or Gray sequence
- Increments either +1 or -2
- Counts up or holds count value

3-bit Up/Down Counter

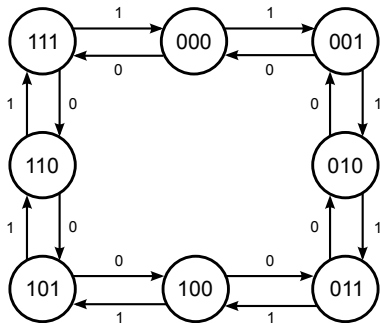

3-bit Up/Down Counter

Present State			Input	Next State		
Q_2	Q_1	Q_0	U	Q_2^+	Q_1^+	Q_0^+
0	0	0	0	1	1	1
0	0	0	1	0	0	1
0	0	1	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	0	1	1
0	1	1	0	0	1	0
0	1	1	1	1	0	0
1	0	0	0	0	1	1
1	0	0	1	1	0	1
1	0	1	0	1	0	0
1	0	1	1	1	1	0
1	1	0	0	1	0	1
1	1	0	1	1	1	1
1	1	1	0	1	1	0
1	1	1	1	0	0	0

3-bit Up/Down Counter

$$Q_2^+ = Q_2'Q_1'Q_0'U' + Q_2'Q_1Q_0U + Q_2Q_1Q_0' + Q_2Q_0U' + Q_2Q_1'U$$

$$Q_1^+ = Q_1'Q_0'U' + Q_1'Q_0U + Q_1Q_0'U + Q_1Q_0U'$$

$$Q_0^+ = Q_0'$$

Several ways to realize the design:

- Logic gates: complex wiring
- Mux
- Decoder
- ROM
- Behavioral Verilog: easiest

How to Design a Sequence Detector


- Start with the expected sequence first.
- Assert the output at the last state.
- Add exit arrows to cover all possible transitions.
 - Each state must have two exit arrows.

110 Sequence Detector

110 Sequence Detector: Moore


IN : 1 1 0 0 0 1 1 0 1 1 1 1 0
 OUT : 0 0 1 0 0 0 0 1 0 0 0 0 1

State	Meaning
S_0	No matching bits yet
S_1	1 (first bit) found
S_2	1 (second bit) found
S_3	0 (third bit) found, assert output

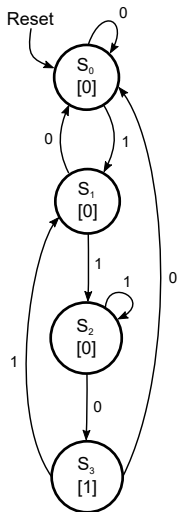

110 Sequence Detector

110 Sequence Detector: Moore

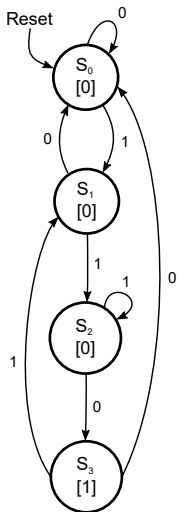


State Encoding	
Symbolic	Encoded
S0	00
S1	01
S2	10
S3	11

Present State		Input	Next State		Output
Q_1	Q_0	x	Q_1^+	Q_0^+	z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	1	1	0
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	0	1	1

110 Sequence Detector

110 Sequence Detector: Moore

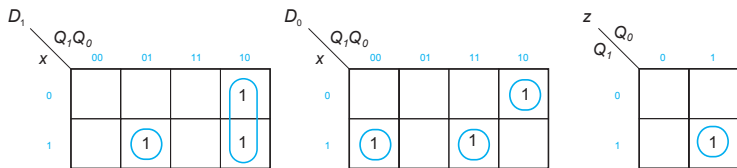

$$D_1 = Q_1 Q_0' + Q_1' Q_0 x$$

$$D_0 = Q_1' Q_0' x + Q_1 Q_0' x' + Q_1 Q_0 x$$

$$z = Q_1 Q_0$$


110 Sequence Detector

110 Sequence Detector: Moore

$$D_1 = Q_1 Q'_0 + Q'_1 Q_0 x$$

$$D_0 = Q'_1 Q'_0 x + Q_1 Q'_0 x' + Q_1 Q_0 x$$


$$z = Q_1 Q_0$$

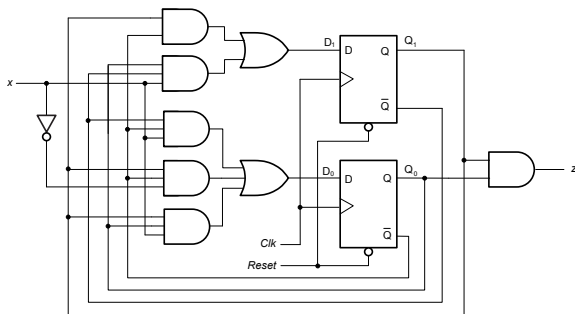

110 Sequence Detector


110 Sequence Detector: Mealy

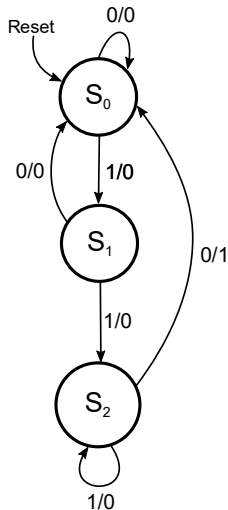IN : 1 1 0 0 0 1 1 0 1 1 1 1 0
 OUT : 0 0 1 0 0 0 0 1 0 0 0 0 1



110 Sequence Detector

110 Sequence Detector: Mealy



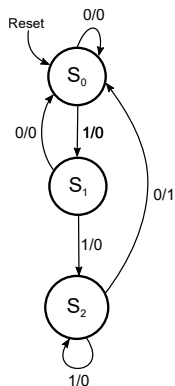


State Encoding	
Symbolic	Encoded
S0	00
S1	01
S2	10
S3	11

Present State		Input	Next State		Output
Q_1	Q_0	x	Q_1^+	Q_0^+	z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	X	X	X
1	1	1	X	X	X

110 Sequence Detector

110 Sequence Detector: Mealy

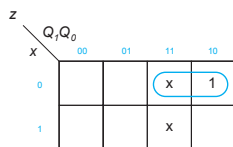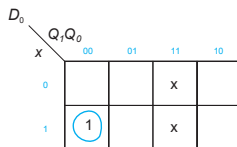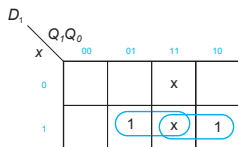

$$D_1 = Q_1x + Q_0x$$


$$D_0 = Q_1'Q_0'x$$

$$z = Q_1x'$$

Alternating Input Detector

010 or 101 Detector

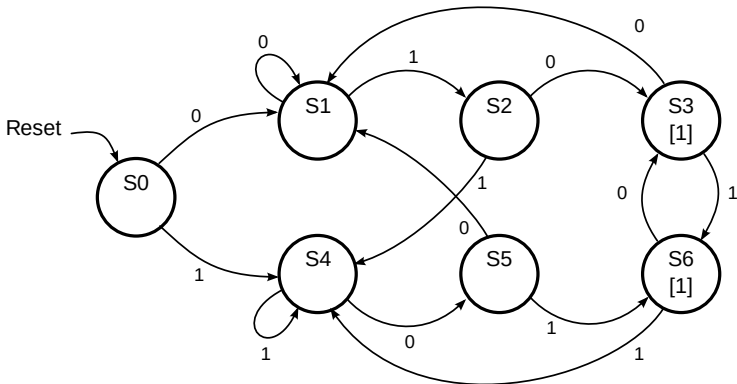X : 0 1 0 0 0 1 0 1 0 1 0 1 0 1 1 1 0 0 1 1 0
 Z : 0 0 1 0 0 0 0 1 0 0 0 1 1 0 0 0 0 0 0 0 0



010 or 101 detector

Present State			Input	Next State			Output
Q_2	Q_1	Q_0	x	Q_2^+	Q_1^+	Q_0^+	z
0	0	0	0	0	0	1	0
			1	1	0	0	
0	0	1	0	0	0	1	0
			1	0	1	0	
0	1	0	0	0	1	1	0
			1	1	0	0	
0	1	1	0	0	0	1	1
			1	1	1	0	
1	0	0	0	1	0	1	0
			1	1	0	0	
1	0	1	0	0	0	1	0
			1	1	1	0	
1	1	0	0	0	1	1	1
			1	1	0	0	
1	1	1	X	X	X	X	X