

# Chapter 14

## FSM with Datapath

### SKEE2263 Digital Systems

Mun'im Zabidi {munim@utm.my}  
Ismahani Ismail {ismahani@fke.utm.my}  
Izam Kamisian {e-izam@utm.my}

Faculty of Electrical Engineering, Universiti Teknologi Malaysia

April 30, 2018


# Table of Contents

**1** FSMD

**2** Ones Counter

**3** Bit-Serial Adder

# FSMD High Level Block Diagram

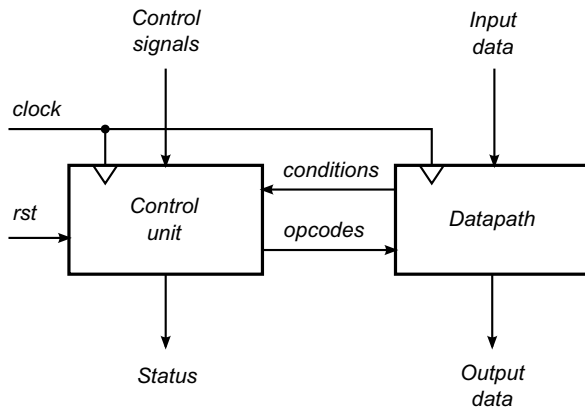

- FSMD = Finite State Machine with Datapath
- a.k.a. CU+DU

## FSMD Components: Datapath Unit (DU)

The Datapath Unit (DU):

- Executes arithmetic and logic functions.
- Typically consists of
  - Registers to store variable of the algorithm
  - ALU and other combinational blocks that implement operation (operators) of the algorithm
  - Step counters that implement the loop counters.
  - Steering logic (multiplexers and buses)

## FSMD Components: Control Unit (DU)


The Control Unit (CU):

- Generates control signals for data path operation.
  - Implemented as an FSM that may be designed in the conventional manner.
  - Receives status signals from data path (e.g. “operation complete”) and from outside world (e.g. “data ready”)
  - Generates two types of signals: opcodes to blocks of datapath, and status signals to the outside world


# FSMD Modeling

- FSMD can be simple to very complex. Use the appropriate modeling tools.
  - State diagrams are usable for simple FSMDs.
  - Algorithmic State Machines (ASMs) almost like state diagram, but looks like flowcharts. Therefore, they can describe more complex decision making sequence.
  - Register Transfer Language (RTL) models how data is transferred from one place to another in a system.
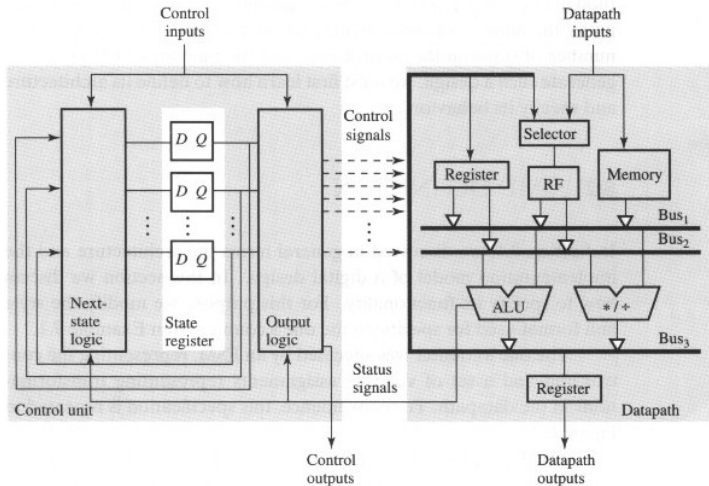
# FSMD RTL View: Example of a Complex System




# Designing a Complex Digital System

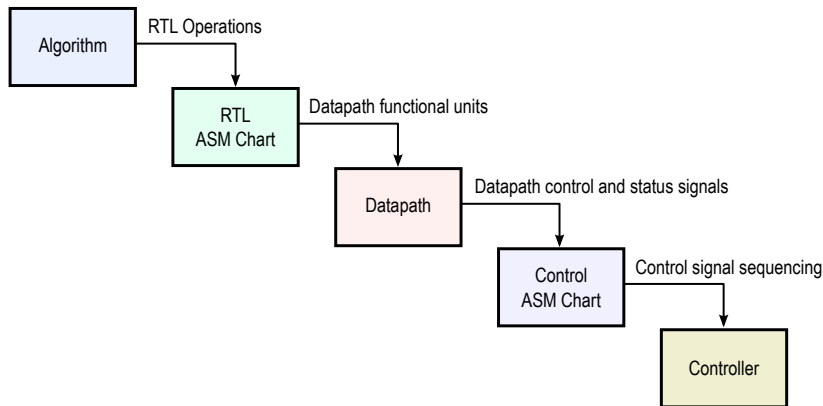




# Ones Counter Entity and Algorithm

 


```
int onescount(unsigned data)
{
    unsigned count = 0;    // reset counter
    while( data != 0 ) {  // repeat as long as data has 1s
        if( data & 1 == 1 ) // if lsb = 1 then bump counter
            count++;
        data = data >> 1;  // shift data for next bit
    }
    return count;
}
```

# Ones Counter Functional Block Diagram

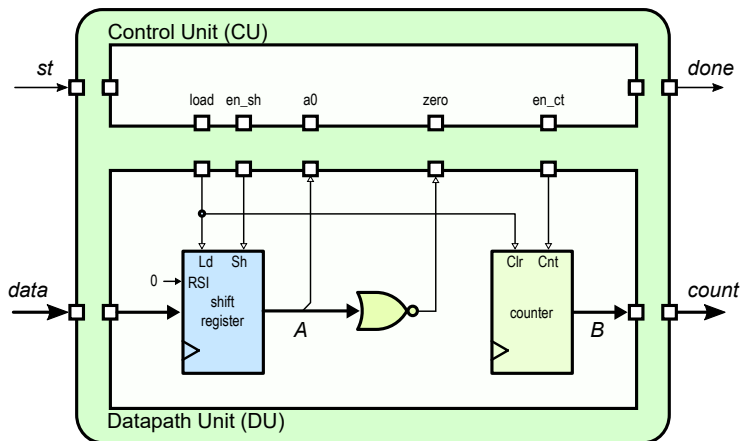

# High-Level ASM Chart

 


## Building Blocks


Some components must specially-designed.

- Up-counter with **clear** and (count) **enable** controls
- Shift register with **load** and (shift) **enable** controls

 
Test the function of each block before integrating into system.




# Low-Level ASM Chart

 

# Ones Counter Simulation

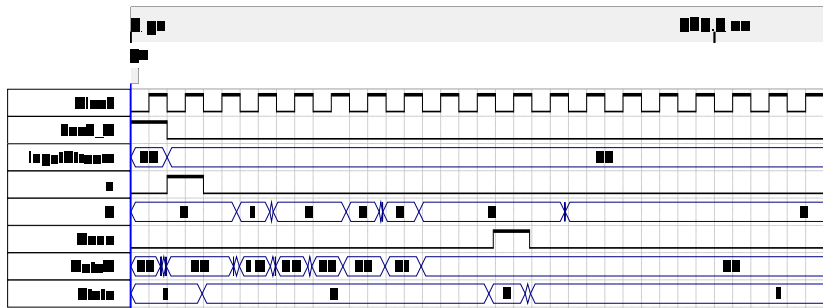

# Serial Adder Entity

 


# Serial Adder Specs

| External Inputs      |  |
|----------------------|--|
| Signal               | Function   |
| <b>A</b>             | First $n$ -bit Operand (Addend)  |
| <b>B</b>             | Second $n$ -bit Operand (Augend)   |
| <b>st</b>            | Start signal which initiates the addition operation  |
| <b>rst</b>           | <i>Puts the controller into the initial state. This signal is used <b>only</b> on system power-up or system lock-up.</i> |
| <b>clk</b>           | <i>Clock signal.</i>   |
| External Outputs     |  |
| <b>S</b>             | The $n$ -bit sum of $S = A + B$  |
| <b>C<sub>4</sub></b> | The carry from $S = A + B$   |
| <b>done</b>          | Active when the operation is complete  |




# Serial Adder Basic Circuit

 

| $A$  | $B$  | $S$  | $s_i$ | $c_{out}$ |
|------|------|------|-------|-----------|
| 1011 | 0011 | 0000 | 0     | 1         |
| 0101 | 0001 | 1000 | 1     | 1         |
| 0010 | 0000 | 1100 | 1     | 0         |
| 0001 | 0000 | 1110 | 1     | 0         |


## Serial Adder Basic Circuit

 

Must add extra circuits to:

- Clear carry flip-flop before adding first set of bits
- Stop clocking when all bits have added

## Datapath

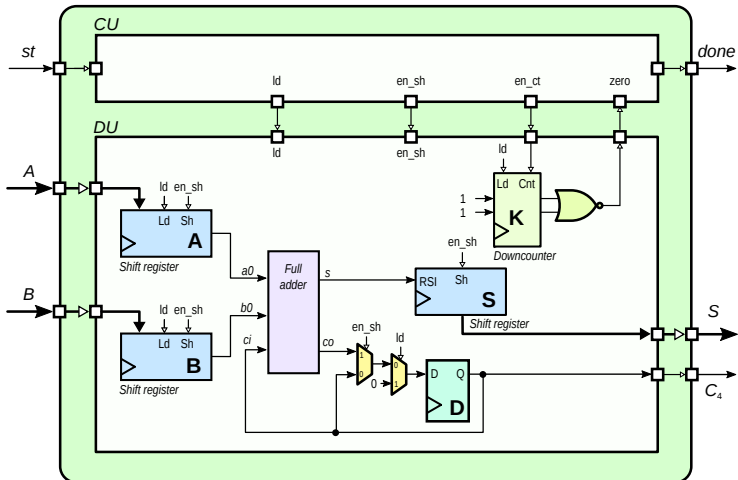

## Signals to Control the Datapath

| Signal       | Function                       |
|--------------|--------------------------------|
| <b>ld</b>    | load the register/counter      |
| <b>en_sh</b> | enable shifting of A, B, S & D |
| <b>en_ct</b> | enable counter K counting      |
| <b>zero</b>  | high when counter K = 0        |


| Datapath |          |          |                      |                        | Control Signals |    |       |       |      |      |
|----------|----------|----------|----------------------|------------------------|-----------------|----|-------|-------|------|------|
| <i>A</i> | <i>B</i> | <i>S</i> | <i>s<sub>i</sub></i> | <i>C<sub>out</sub></i> | st              | ld | en_sh | en_ct | zero | done |
| 1011     | 0011     | xxxx     | 0                    | 1                      | 0               | 1  | 0     | 0     | 0    | 0    |
| 1011     | 0011     | xxxx     | 0                    | 1                      | 1               | 1  | 0     | 0     | 0    | 0    |
| 0101     | 0001     | 0xxx     | 1                    | 1                      | 1               | 0  | 1     | 1     | 0    | 0    |
| 0010     | 0000     | 10xx     | 1                    | 0                      | 1               | 0  | 1     | 1     | 0    | 0    |
| 0001     | 0000     | 110x     | 1                    | 0                      | 1               | 0  | 1     | 1     | 1    | 0    |
| 0000     | 0000     | 1110     | 0                    | 0                      | 1               | 0  | 0     | 0     | 0    | 1    |

## Datapath Operation

- On reset, flip-flop D is cleared
- Idle state, waiting for *st* (start) signal: A, B registers and counter C are continuously loaded. Flip-flop D remains cleared as it is not enabled.
- When start signal is received, repeat the following 4 times:
  - Shift registers A, B, S and flip-flop D
  - Decrement counter C
- After the bits have been shifted 4 times (signaled by Zero signal from downcounter), stop shifting and output the *done* signal. The 5-bit sum is now stable and can be used by other circuits.



# High-Level ASM Chart

Describes what the circuit is doing

 


# Building Blocks: DFF with enable & load

Special circuits designed at low level

  

# Building Blocks: SRG with Parallel Load


Special circuits designed at low level

 




# Building Blocks: Loop Control Downto

Special circuits designed at low level

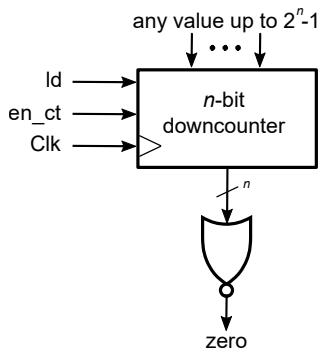

# Low-Level ASM Chart

Sequences the control signals

 

# Serial Adder Simulation

