

# Chapter 9

## Introduction to Finite State Machines

### SKEE2263 Digital Systems

Mun'im/Ismahani/Izam


FEE, Universiti Teknologi Malaysia

April 19, 2016

# Table of Contents

- 1 FSM Modeling
- 2 FSM Design
- 3 Moore FSM
- 4 Mealy FSM
- 5 Moore vs Mealy
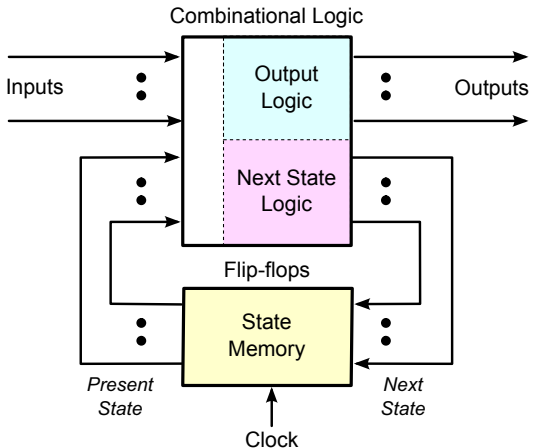
# General Structure of Finite State Machines (FSM)




## Components & Types

Components:

- **State memory** to store *present state* and has  $2^n$  distinct states which  $n$  represents the number of flip-flops used.
- **Next state logic** to determine the *next state* when state transition occurs.
- **Output logic** to determine the output as a function of current state and inputs.


Two widely known types of FSM models are Mealy and Moore.

## General Structure of Moore FSM

 


- **Moore model:** The output depends on the present state *only*.

## General Structure of Mealy FSM


 


- **Mealy model:** The output depends on the present state *and* the present inputs.

# FSM Timing

 

# State Diagrams

  



# State Tables

**Moore Symbolic State Table**

Present State	Input	Next State	Output	Comments
	A		B	
A	0	A	0	Remain idle in starting state
	1	B		Go to next state
B	0	A	1	Go back to starting state
	1	B		Remain in current state

**Mealy Symbolic State Table**

Present State	Input	Next State	Output	Comments
	A		B	
A	0	A	0	Remain idle in starting state
	1	B	0	Go to next state
B	0	A	1	Go back to starting state
	1	B	0	Remain in current state


# State Encoding

No	Binary	Gray	Johnson	One-Hot	Almost One-Hot
0	000	000	0000	00000001	0000000
1	001	001	0001	00000010	0000001
2	010	011	0011	00000100	0000010
3	011	010	0111	00001000	0000100
4	100	110	1111	00010000	0001000
5	101	111	1110	00100000	0010000
6	110	101	1100	01000000	0100000
7	111	100	1000	10000000	1000000


# FSM Design Procedure

- 1 Conceptualize – Understand the statement of the specification:
  - Define all **inputs** and **outputs**
  - Determine system constraints
- 2 Translate the concept into a **state diagram**:
  - Determine the **number of states** required by the system
  - Determine the required **transitions**
- 3 **Assign** a unique binary number to each state.
- 4 Create the **state table**.
- 5 Extract the **equations**: Express the logic circuits as Boolean equations.
- 6 **Implement** the FSM: Enter and verify the design.


# Level to Pulse Converter Top Level

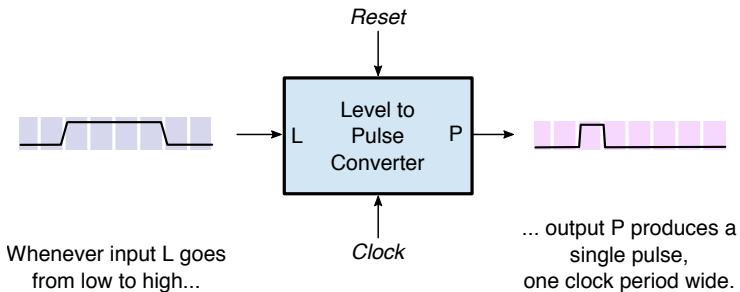

# Level to Pulse Converter Block Diagram

 
 
# Level to Pulse Converter Moore State Diagram



## Level to Pulse Converter State Table

Present State		In	Next State		Out	Comments
$Q_1$	$Q_0$	$L$	$Q_1^+$	$Q_0^+$	$P$	
0	0	0	0	0	0	Waiting for rising edge
0	0	1	0	1	0	
0	1	0	0	0	1	Edge detected
0	1	1	1	1	1	
1	1	0	0	0	0	Waiting for falling edge
1	1	1	1	1	0	

# Level to Pulse Converter Kmaps

		$L$	
		0	1
$Q_1Q_0$	00		
	01		1
	11		1
	10	x	x

$$Q_1^+ = LQ_0$$

		$L$	
		0	1
$Q_1Q_0$	00		1
	01		1
	11		1
	10	x	x


$$Q_0^+ = L$$

		$Q_0$	
		0	1
$Q_1$	0		1
	1	x	


$$P = Q_1'Q_0$$



 
# Level to Pulse Converter Schematic: Moore Type


 
# Level to Pulse Converter Moore Alternate State Diagram


 
# Level to Pulse Converter Mealy State Diagram




## Level to Pulse Converter Mealy State Table

Current State	In	Next State	Out	Comments
$Q$	$L$	$Q^+$	$P$	
0	0	0	0	Waiting for rising edge
0	1	1	1	
1	0	0	0	Waiting for falling edge
1	1	1	0	

$$Q^+ = L$$


$$P = Q'L$$
 
## Level to Pulse Converter Schematic: Mealy Type


 
# Moore vs Mealy

- Mealy: output =  $f(\text{state, inputs})$
- Moore: output =  $f(\text{state only})$



Moore vs Mealy level to pulse converter.

# Synchronous Mealy

- Mealy responds to inputs faster than Moore, but...
- Mealy has glitchy outputs
  - outputs can change in the middle of a clock period
  - i.e. asynchronous outputs
- Solution: pass the output through a register

