

# Chapter 10

## Finite State Machines Synthesis

### SKEE2263 Digital Systems

Mun'im/Ismahani/Izam

FEE, Universiti Teknologi Malaysia

April 15, 2016

# Table of Contents

- 1 Design Process
- 2 Single-Mode Counters
- 3 Multimode Counters
- 4 Sequence Detectors
- 5 Multi-Sequence Detectors

# FSM Design Process

Step	Description
<i>Conceptualize</i>	Understand the statement of the specification.
<i>Capture the FSM</i>	Translate the problem into state diagram. Determine the number of <b>states</b> required, <b>inputs</b> , <b>outputs</b> and state <b>transitions</b> .
<i>Encode the states</i>	Assign a unique binary number to each state.
<i>Create the state table</i>	Create a truth table for the combinational logic for <b>next state</b> generation and <b>output</b> decoding.
<i>Extract the equations</i>	Express the logic circuits as Boolean equations.
<i>Implement the FSM</i>	Enter and verify the design.

# Counters


- Definition of counters:
  - Starts from a particular state
  - Goes thru fixed sequence of states
  - Returns to initial state
  - Repeats indefinitely
- Most counters (but not all) are Medvedev state machines
  - Medvedev machine have not output logic.
  - Register outputs = system outputs.
- Single-mode counters:
  - The only input is the clock signal
- Multi-mode counters:
  - Has input to select mode of operation

## 2-bit Binary Counter
 
### Binary Counters

$n$  state variables  $\Rightarrow 2^n$  sequential states

Binary 2-bit counter : straight binary sequence  $0 \rightarrow 1 \rightarrow 2 \rightarrow 3 \rightarrow 0$




Present State		Next State	
$Q_1$	$Q_0$	$Q_1^+$	$Q_0^+$
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

## 2-bit Binary Counter

Present State		Next State	
$Q_1$	$Q_0$	$Q_1^+$	$Q_0^+$
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0


$$Q_1^+ = Q_1 \oplus Q_0$$

$$Q_0^+ = Q_0'$$

 
 
## Counter with Arbitrary Sequence

- Counter next states can be non-sequential
- Number of states can be  $< 2^n$
- All valid:
  - $0 \rightarrow 3 \rightarrow 1 \rightarrow 2 \rightarrow 0$ ,
  - $0 \rightarrow 1 \rightarrow 3 \rightarrow 2 \rightarrow 0$ ,
  - $0 \rightarrow 1 \rightarrow 3 \rightarrow 0$




# Counter with Arbitrary Sequence

Present State		Next State	
$Q_1$	$Q_0$	$Q_1^+$	$Q_0^+$
0	0	0	1
0	1	1	1
1	0	×	×
1	1	0	0

$$Q_1^+ = Q_1' Q_0$$

$$Q_0^+ = Q_1'$$

 



# Definition


## Multi-Mode Counter

A counter whose counting sequence depends not only on the clock but also on some other control signal(s).

Examples:

- Counts up or down
- Counts in binary or Gray sequence
- Increments either +1 or -2
- Counts up or holds count value

## 3-bit Up/Down Counter

 

# 3-bit Up/Down Counter

Present State			Input	Next State		
$Q_2$	$Q_1$	$Q_0$	$U$	$Q_2^+$	$Q_1^+$	$Q_0^+$
0	0	0	0	1	1	1
0	0	0	1	0	0	1
0	0	1	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	0	1	1
0	1	1	0	0	1	0
0	1	1	1	1	0	0
1	0	0	0	0	1	1
1	0	0	1	1	0	1
1	0	1	0	1	0	0
1	0	1	1	1	1	0
1	1	0	0	1	0	1
1	1	0	1	1	1	1
1	1	1	0	1	1	0
1	1	1	1	0	0	0

## 3-bit Up/Down Counter

$$Q_2^+ = Q_2'Q_1'Q_0'U' + Q_2'Q_1Q_0U + Q_2Q_1Q_0' + Q_2Q_0U' + Q_2Q_1'U$$

$$Q_1^+ = Q_1'Q_0'U' + Q_1'Q_0U + Q_1Q_0'U + Q_1Q_0U'$$

$$Q_0^+ = Q_0'$$

Several ways to realize the design:

- Logic gates: complex wiring
- Mux
- Decoder
- ROM
- Behavioral Verilog: easiest


# How to Design a Sequence Detector

- Start with the expected sequence first.
- Assert the output at the last state.
- Add exit arrows to cover all possible transitions.
  - Each state must have two exit arrows.


# 110 Sequence Detector: Moore

IN : 1 1 0 0 0 1 1 0 1 1 1 1 0  
 OUT : 0 0 1 0 0 0 0 1 0 0 0 0 1

State	Meaning
$S_0$	No matching bits yet
$S_1$	1 (first bit) found
$S_2$	1 (second bit) found
$S_3$	0 (third bit) found, assert output

 



# 110 Sequence Detector: Moore

 

State Encoding	
Symbolic	Encoded
S0	00
S1	01
S2	10
S3	11

Present State		Input	Next State		Output
$Q_1$	$Q_0$	$x$	$Q_1^+$	$Q_0^+$	$z$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	1	1	0
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	0	1	1

# 110 Sequence Detector: Moore

  

$$D_1 = Q_1 Q'_0 + Q'_1 Q_0 x$$

$$D_0 = Q'_1 Q'_0 x + Q_1 Q'_0 x' + Q_1 Q_0 x$$

$$z = Q_1 Q_0$$




# 110 Sequence Detector: Moore

$$D_1 = Q_1 Q'_0 + Q'_1 Q_0 x$$


$$D_0 = Q'_1 Q'_0 x + Q_1 Q'_0 x' + Q_1 Q_0 x$$

$$z = Q_1 Q_0$$

 

 
# 110 Sequence Detector: Mealy

IN : 1 1 0 0 0 1 1 0 1 1 1 1 0  
 OUT : 0 0 1 0 0 0 0 1 0 0 0 0 1





# 110 Sequence Detector: Mealy

 

State Encoding	
Symbolic	Encoded
S0	00
S1	01
S2	10
S3	11

Present State		Input	Next State		Output
$Q_1$	$Q_0$	$x$	$Q_1^+$	$Q_0^+$	$z$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	X	X	X
1	1	1	X	X	X

# 110 Sequence Detector: Mealy

  


$$D_1 = Q_1x + Q_0x$$

$$D_0 = Q_1'Q_0'x$$

$$z = Q_1x'$$
 
## 00-then-11 Detector

- Detect 00 followed by any sequence ending with 11.
- 11 can follow 00 immediately, or after any number of bits.
- Output 1 for exactly one clock cycle
- Let us use Gray state encoding.



## 00-then-11 detector

Present State			Input $x$	Next State			Output $y$
$Q_2$	$Q_1$	$Q_0$		$Q_2^+$	$Q_1^+$	$Q_0^+$	
0	0	0	0	0	0	1	0
			1	0	0	0	
0	0	1	0	0	1	1	0
			1	0	0	0	
0	1	0	0	0	1	1	0
			1	1	1	0	
0	1	1	0	0	1	1	0
			1	0	1	0	
1	0	0	X	X	X	X	X
1	0	1	X	X	X	X	X
1	1	0	0	0	0	1	1
			1	0	0	0	
1	1	1	X	X	X	X	X

# 00-then-11 Detector

$$Q_2^+ = Q_2' Q_1 Q_0' x$$

$$Q_1^+ = Q_2' Q_1 + Q_0 x'$$

$$Q_0^+ = x'$$

$$y = Q_2$$